

Homework/Project 01

EE619A

Submitted by- Group no-26

Rahul Kumar Gupta	21204408	rahulkg21@iitk.ac.in	MS(MVLSI)
Sameer Kumar	21204411	sameerk21@iitk.ac.in	MS(MVLSI)
Sagar	21204409	sagar21@iitk.ac.in	MS(MVLSI)

We have used Tcad software for gate level diagrams and ICARUS as well as Xilinx Vivado for running the code.

Q1.

INPUT BUTTONS : D0,D1,D2,D3,D4,D5,D6,D7,D8,D9

The user gets to select only one of the above mentioned buttons (selecting a button corresponds to logic 1).

By default our outputs will be set to logic low.

The logic for the binary output can be written from the table below

(MSB) B3 = D8 + D9

B2= D7+ D6+ D5+ D4

B1= D7+ D6+ D3+ D2

(LSB) B0= D9+ D7+ D5+ D3+ D1

ENCODER INPUTS										ENCODER OUTPUTS			
D0	D1	D2	D3	D4	D5	D6	D7	D8	D9	B3	B2	B1	B0
0	0	0	0	0	0	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	0	0	0	1	0	0
0	0	0	0	0	1	0	0	0	0	0	1	0	1
0	0	0	0	0	0	1	0	0	0	0	1	1	0
0	0	0	0	0	0	0	1	0	0	0	1	1	1
0	0	0	0	0	0	0	0	1	0	1	0	0	0
0	0	0	0	0	0	0	0	0	1	1	0	0	1

Here is the gate level logic circuit that will output a single digit decimal digit in BCD form:

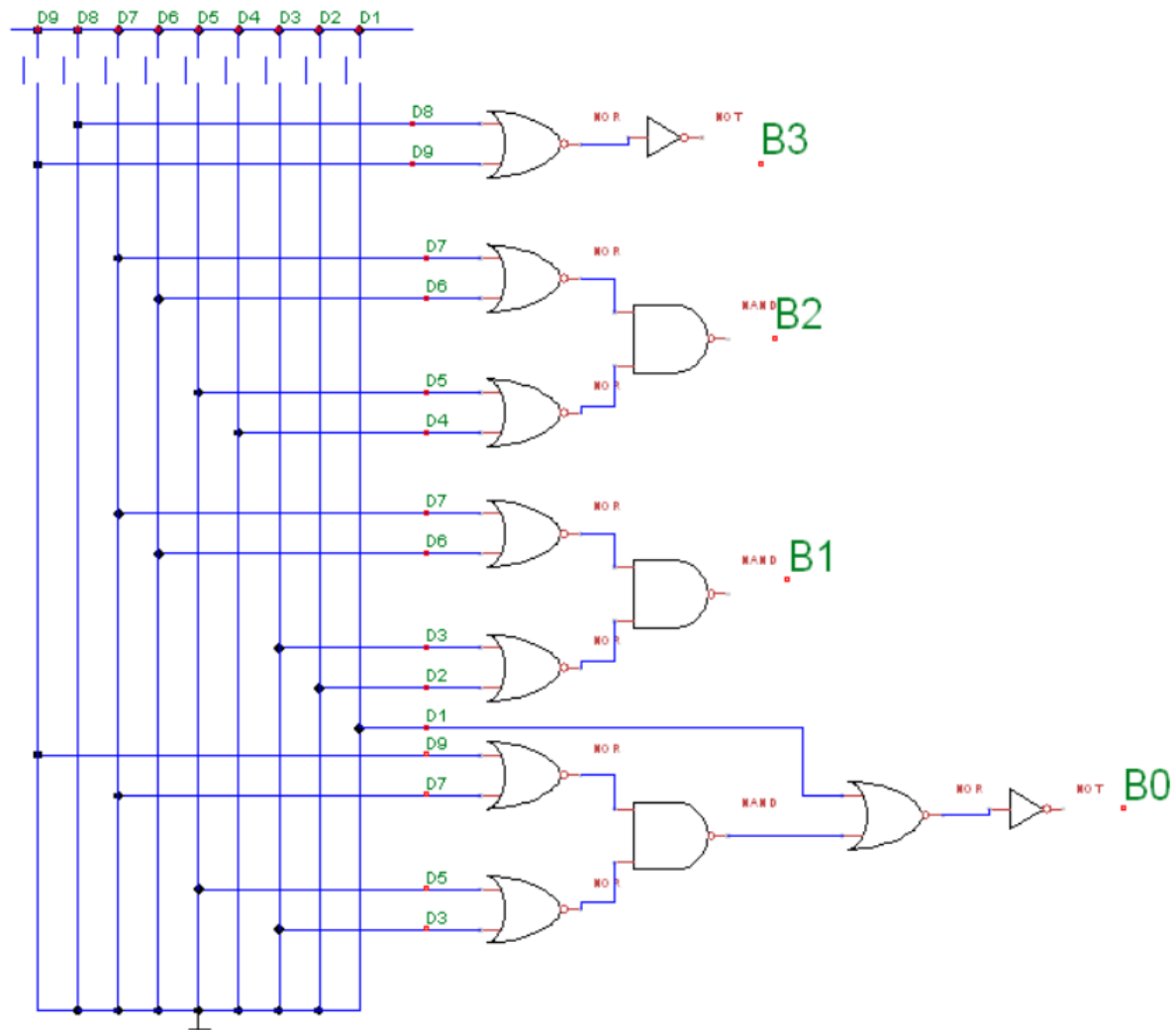


Fig.1. Circuit for converting decimal input to binary output

Q2.

Using the above results we can assume that we have converted decimal into BCD. Therefore we have B3, B2, B1, B0 (B3 is the MSB and B0 is the LSB) as the inputs. a,b,c,d,e,f,g , DP=0(always).

 


Fig.2. A Seven segment display(google images)

Truth table:

BCD INPUTS				OUTPUTS						
B3	B2	B1	B0	A	B	C	D	E	F	G
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	0	0	1	1

From Truth table.

$$a = \sum m(0, 2, 3, 5, 6, 7, 8, 9)$$

$$b = \sum m(0, 1, 2, 3, 4, 7, 8, 9)$$

$$c = \sum m(0, 1, 3, 4, 5, 6, 7, 8, 9)$$

$$d = \sum m(0, 2, 3, 5, 6, 8)$$

$$e = \sum m(0, 2, 6, 8)$$

$$f = \sum m(0, 4, 5, 6, 8, 9)$$

$$g = \sum m(2, 3, 4, 5, 6, 8, 9)$$

Don't care

$$\} + \sum (10, 11, 12, 13, 14, 15)$$

$$\begin{array}{c} B_1, B_0 \\ B_3, B_2 \end{array}$$

1		1	1
	1	1	1
x	x	x	x
1	1	x	x

1	1	1	1
1		1	
x	x	x	x
1	1	x	x

1	1	1	
1	1	1	1
x	x	x	x
1	1	x	x

$$a = \bar{B}_2 \bar{B}_0 + B_1 + B_3 + B_2 B_0$$

$$b = \bar{B}_2 + \bar{B}_1 \bar{B}_0 + B_1 B_0$$

$$c = \bar{B}_1 + B_0 + B_2$$

1		1	1
	1		1
x	x	x	x
1	1	x	x

1			1
			1
x	x	x	x
1		x	x

1			
1	1		1
x	x	x	x
1	1	x	x

$$d = \bar{B}_2 \bar{B}_0 + \bar{B}_2 B_1 + B_2 \bar{B}_1 B_0 + B_1 \bar{B}_0 + B_3$$

$$e = \bar{B}_2 \bar{B}_0 + B_1 \bar{B}_0$$

$$f = \bar{B}_1 \bar{B}_0 + B_2 \bar{B}_1 + B_2 \bar{B}_0 + B_3$$

		1	1
1	1		1
x	x	x	x
1	1	x	x

$$g = \bar{B}_2 B_1 + B_2 \bar{B}_1 + B_3 + B_2 \bar{B}_0$$

$$A = B_1 + B_3 + B_2 \sim B_0$$

$$B = \sim B_2 + B_2 \sim B_0$$

$$C = B_2 + \sim B_1 + B_0$$

$$D = \sim B_2 \sim B_0 + \sim B_2 B_1 + B_2 \sim B_1 B_0 + B_1 \sim B_0 + B_3$$

$$E = \sim B_2 \sim B_0 + B_1 \sim B_0$$

$$F = B_3 + B_2 \sim B_1 + B_2 \sim B_0 + \sim B_1 \sim B_0$$

$$G = B_1 \wedge B_2 + B_3 + B_2 \sim B_0$$

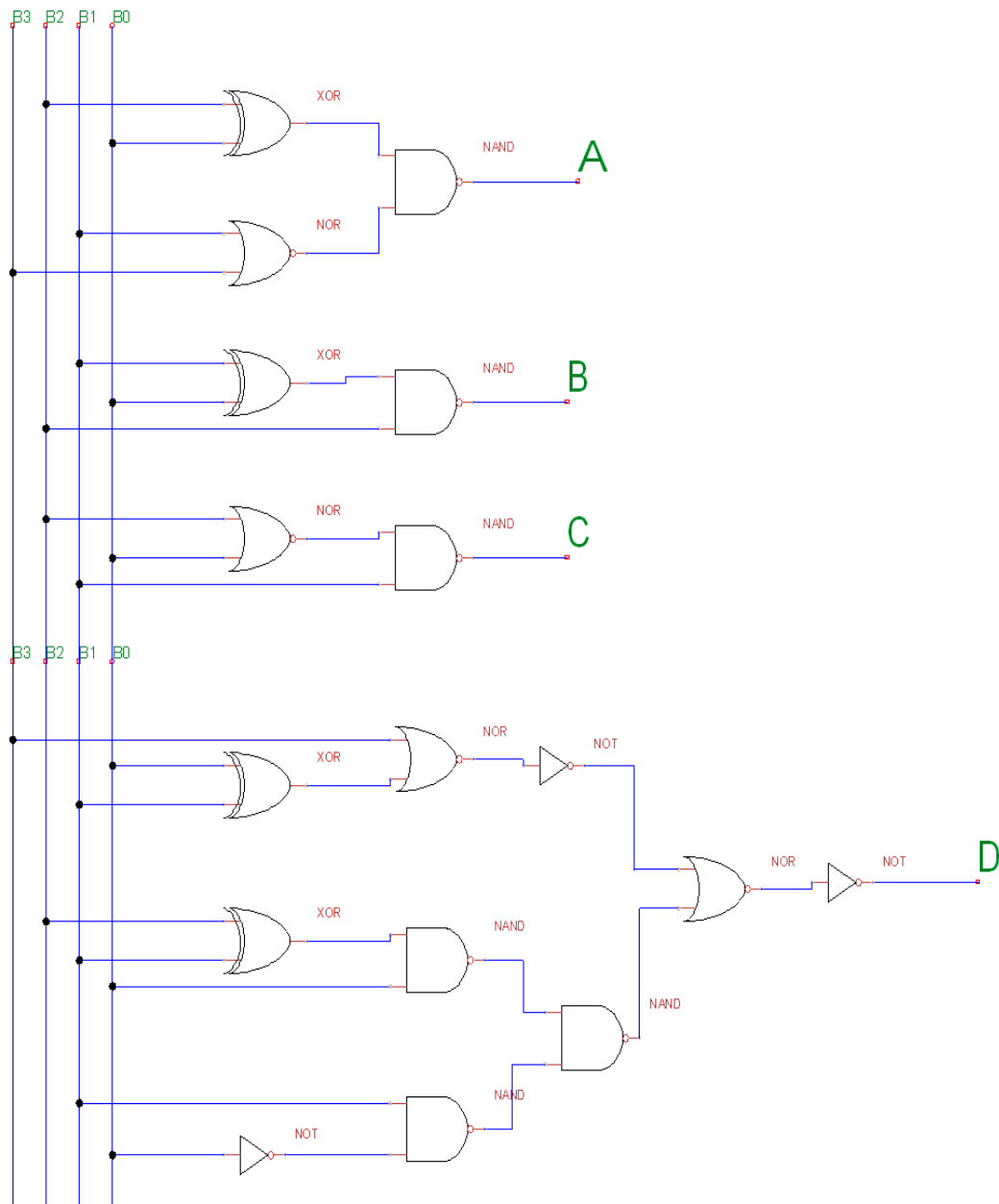


Fig.3. Binary to seven segment logic circuit(A,B,C)

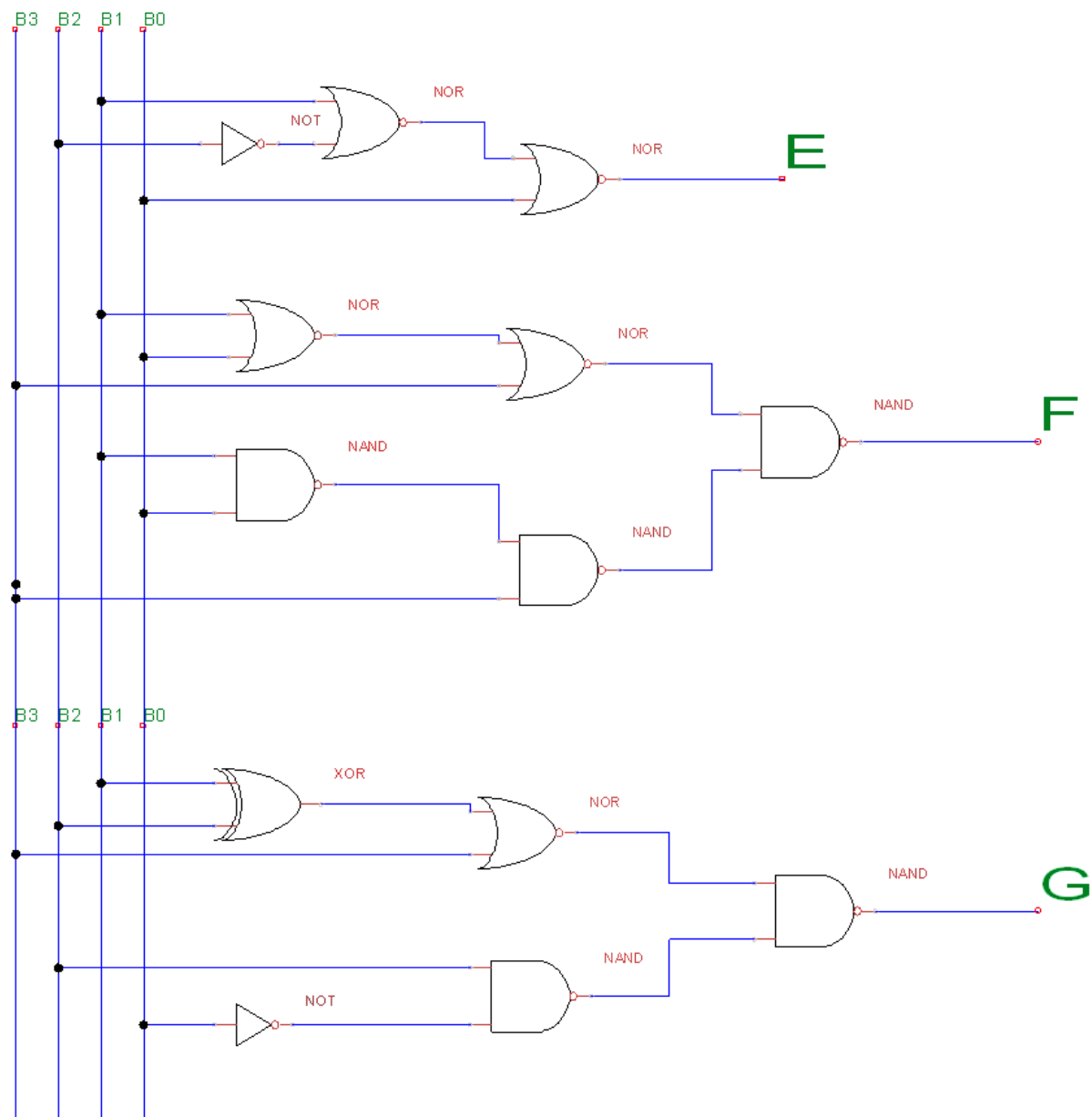


Fig.4. Binary to seven segment logic circuit(D,E,F)

Q3.

Given two decimal integers represented in BCD form x and y.

MSB LSB
 x= X3 X2 X1 X0
 y= Y3 Y2 Y1 Y0

For equality detection bitwise, we can use XNOR gate as it is an equality detector.

Ex: $1 \sim 1 = 1$; $0 \sim 0 = 1$

Since we are dealing with only 0s and 1s then if $A > B$ it means that $A=1$ and $B=0 \rightarrow (A \sim B) = 1$

The above logic is used for inequalities.

x	y	$x > y$	$x = y$	$x < y$
0000	0000	0	1	0
0000	0001	0	0	1
0011	0010	1	0	0
1000	0011	1	0	0
0000	0100	0	0	1
0101	0101	0	1	0
0110	0110	0	1	0
0110	0111	0	0	1
0110	1000	0	0	1
1001	1000	1	0	0

Some of the examples are shown in the table above

Therefore **for $x=y$**

We have $(X3 \sim Y3).(X2 \sim Y2).(X1 \sim Y1).(X0 \sim Y0)$

For $x > y$

We have $(X3 \sim Y3) + (X3 \sim Y3)(X2 \sim Y2) + (X3 \sim Y3).(X2 \sim Y2).(X1 \sim Y1) + (X3 \sim Y3).(X2 \sim Y2).(X1 \sim Y1).(X0 \sim Y0)$

For $x < y$

We have $(Y3 \sim X3) + (Y3 \sim X3)(Y2 \sim X2) + (Y3 \sim X3).(Y2 \sim X2).(Y1 \sim X1) + (Y3 \sim X3).(Y2 \sim X2).(Y1 \sim X1).(Y0 \sim X0)$

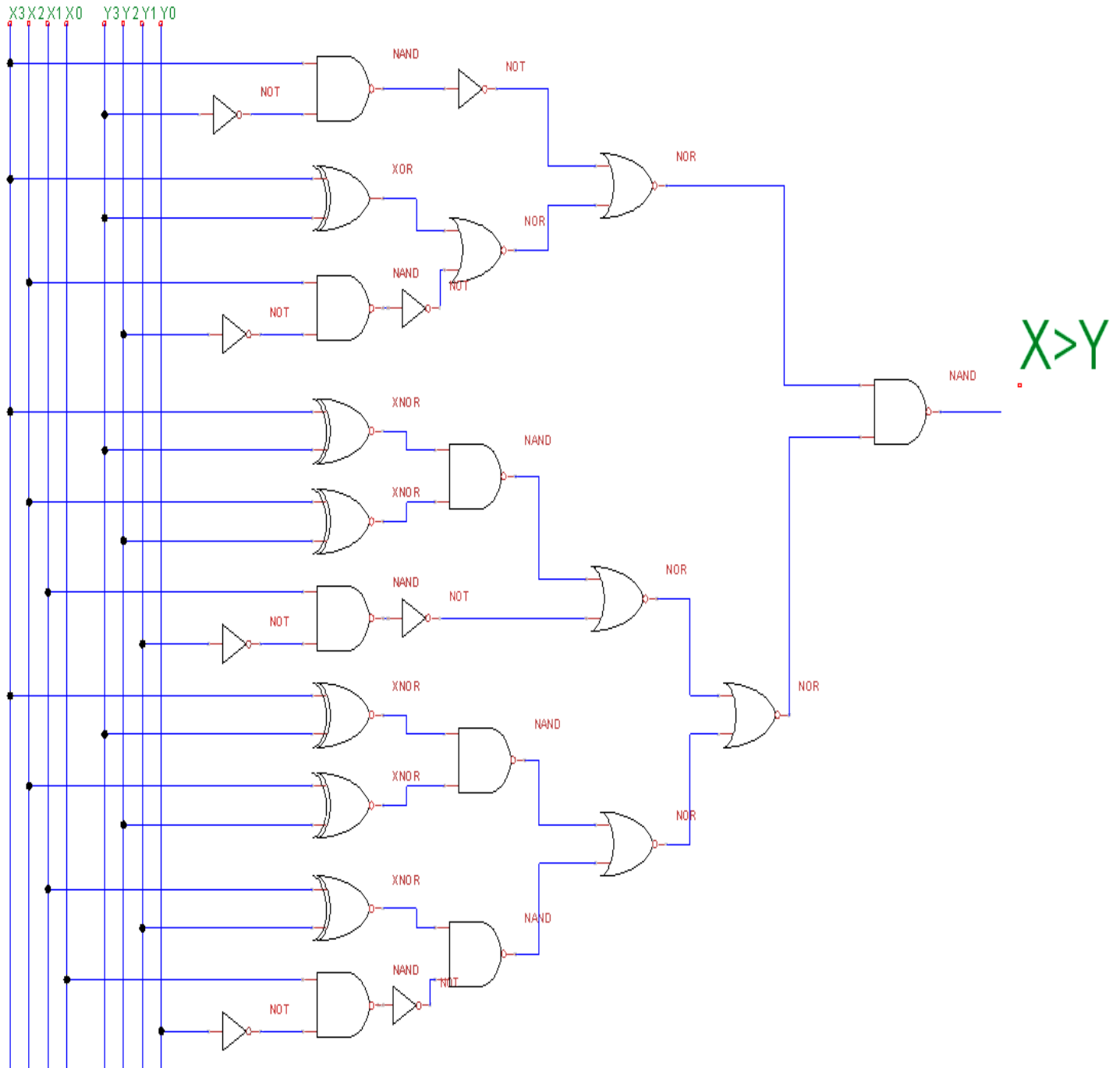


Fig.5. Circuit based on logic provided for $X > Y$

$$X_3 \sim Y_3 + (X_3 \sim Y_3)(X_2 \sim Y_2) + (X_3 \sim Y_3)(X_2 \sim Y_2)(X_1 \sim Y_1) + (X_3 \sim Y_3)(X_2 \sim Y_2)(X_1 \sim Y_1)(X_0 \sim Y_0)$$

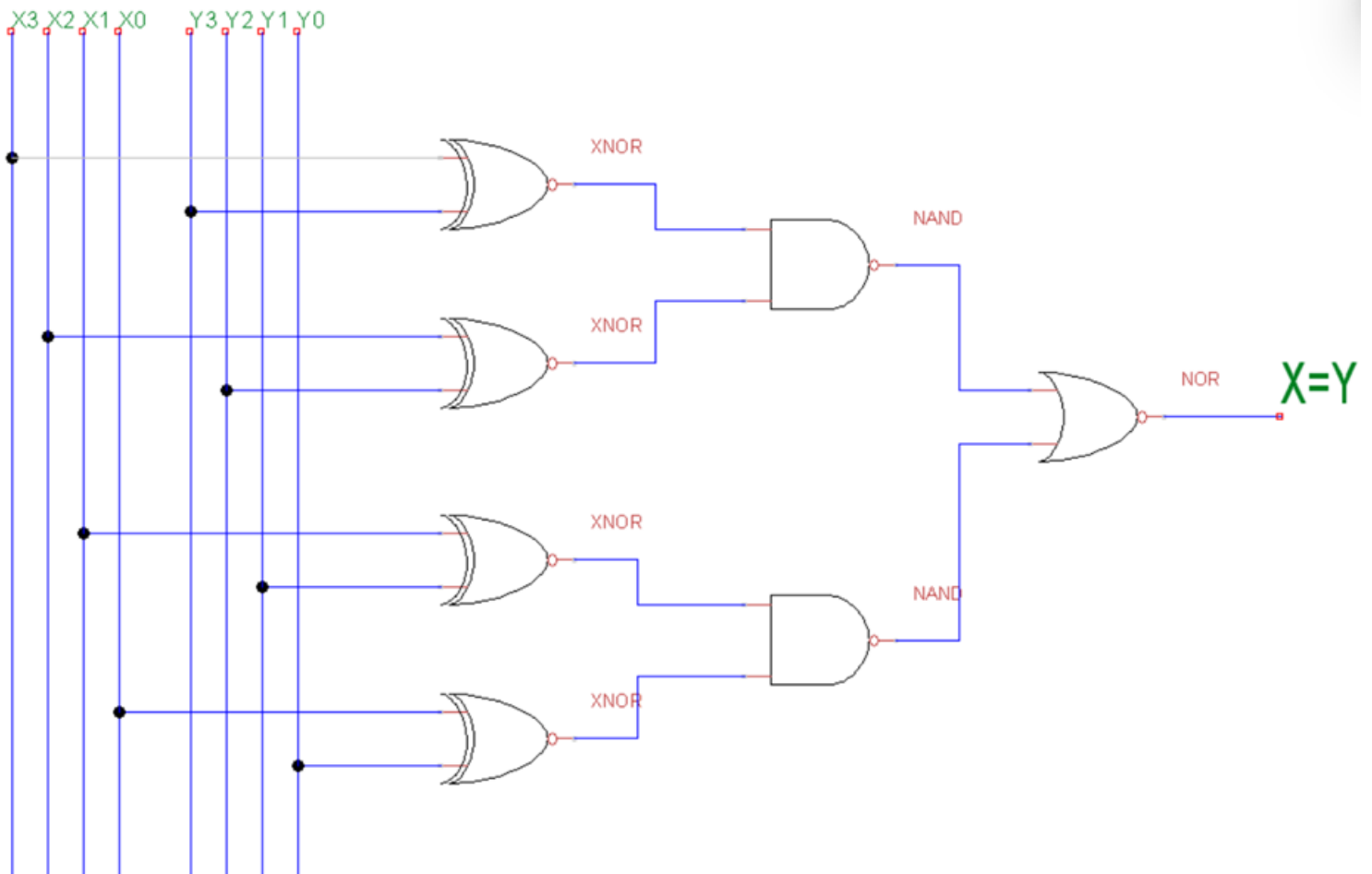


Fig.6. Circuit based on logic provided for $X=Y$

$$(X_3 \sim Y_3) \cdot (X_2 \sim Y_2) \cdot (X_1 \sim Y_1) \cdot (X_0 \sim Y_0)$$

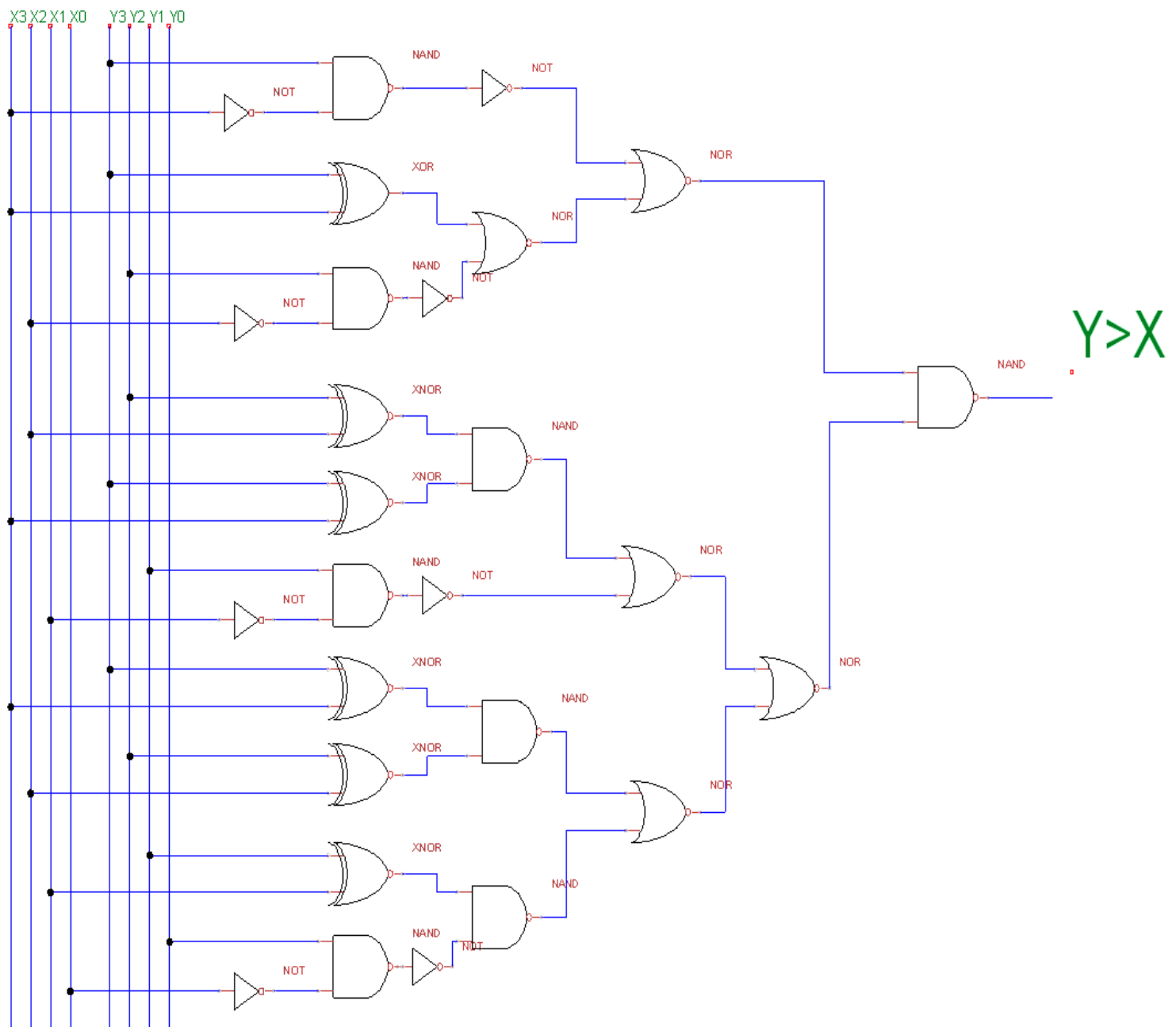


Fig.7. Circuit based on logic provided for $X < Y$

$$(Y_3 \sim X_3) + (Y_3 \sim^X X_3)(Y_2 \sim X_2) + (Y_3 \sim^X X_3)(Y_2 \sim^X X_2)(Y_1 \sim X_1) + (Y_3 \sim^X X_3)(Y_2 \sim^X X_2)(Y_1 \sim^X X_1)(Y_0 \sim X_0)$$

Q4.

Here we'll be using the BCD to 7-segment block designed in Q2.

Here is the gate level logic circuit of a Full Adder

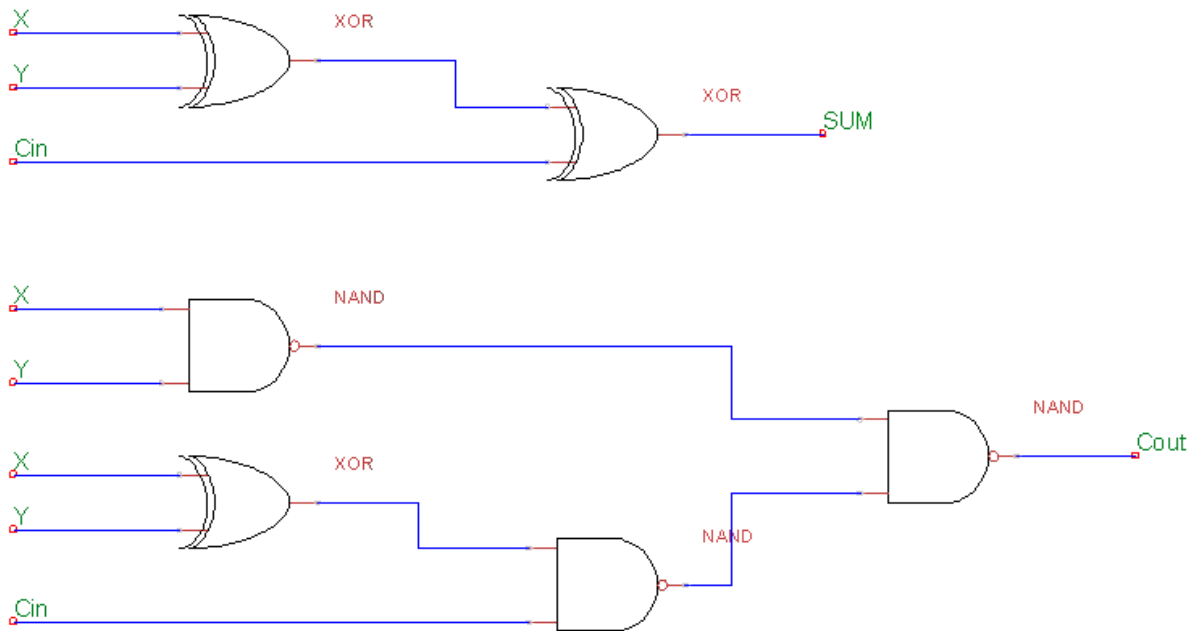


Fig.8. SUM and CARRY based on given condition of question

$$\text{SUM} = X \oplus Y \oplus \text{Cin}$$

$$\text{Cout} = \sim [(\sim(X.Y)).(\sim (X \oplus Y).\text{Cin}))]$$

Above circuit can be modeled as:

 


Fig.9. Block for 1 bit adder

Using the above designed full adder, we can design a 4 bit Full Adder

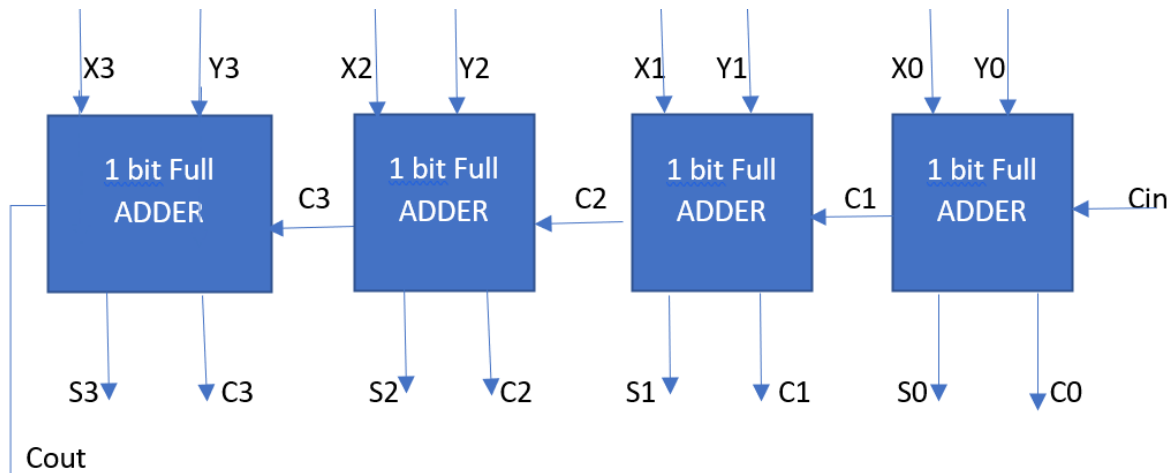


Fig.10. Block for 4 bit adder

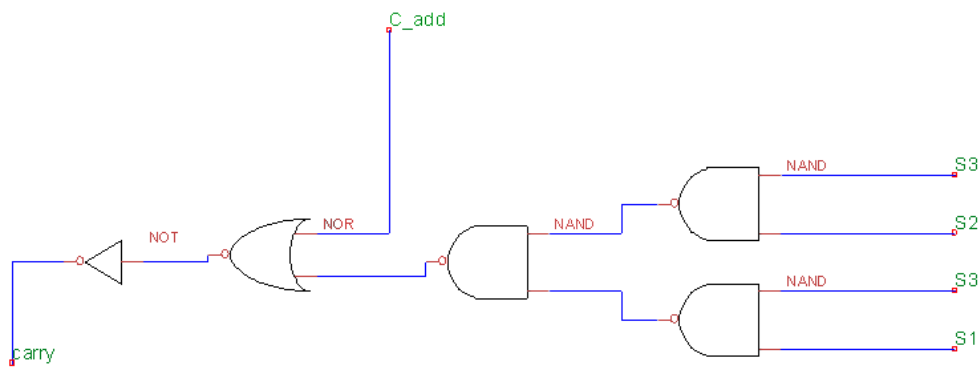


Fig.11. Logic implemented for +6 whenever the 4 bit adder exceeds 9(1001) to convert to BCD

The above circuit is the +6 block that is used to add 6(0110) in the result to convert into BCD(if required).

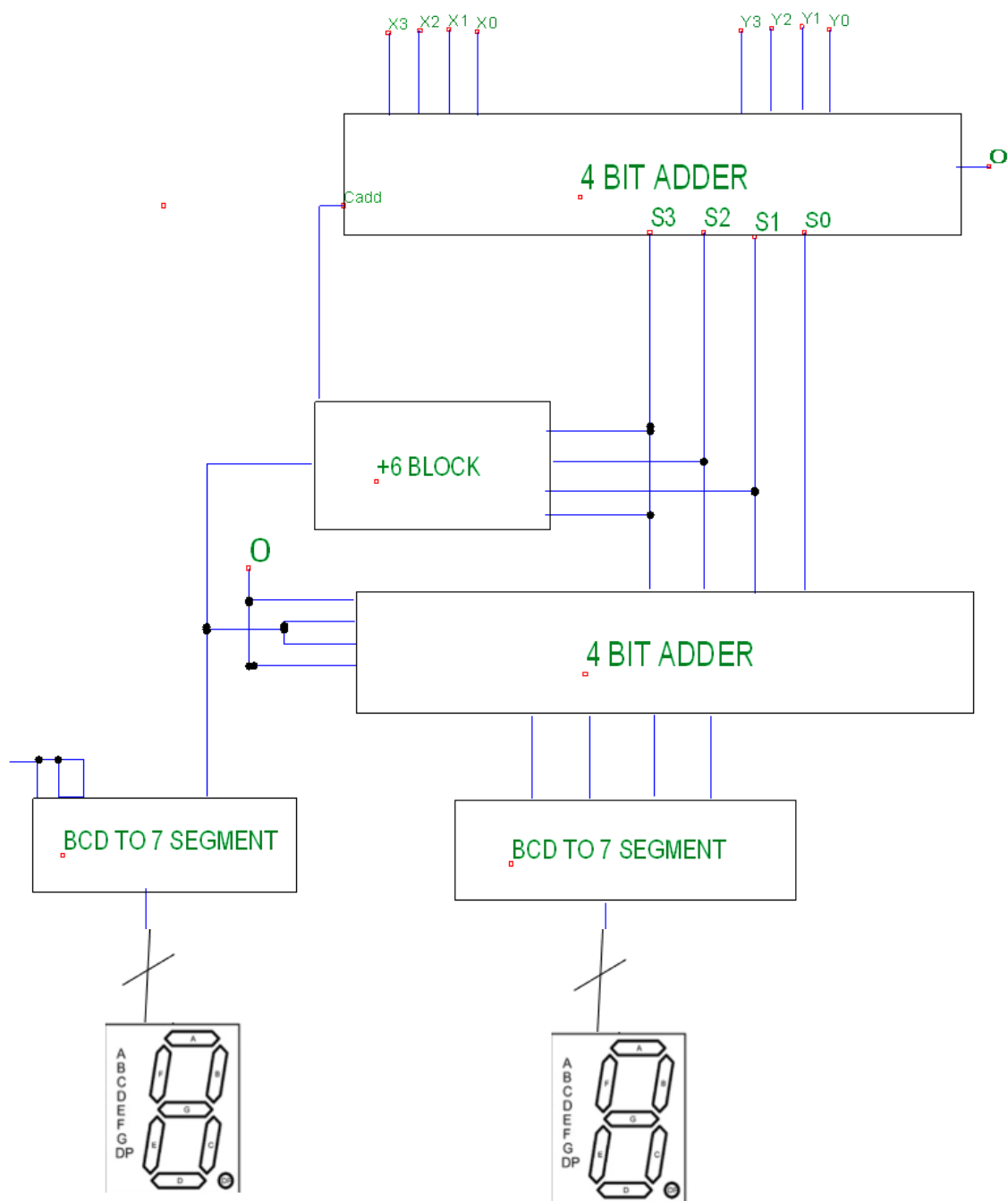


Fig.12. A BCD adder interfacing with 2 seven segment

The BCD to seven segment block is taken from question 2

Q5.

Given two single digit decimal digits x, y such that $(x \geq y \geq 0)$

We have to perform $x - y$ always.

Both x and y are in five bit binary form but since both of them are positive and have value less than 10 therefore the fifth bit is always zero.

The subtraction scheme used is that of 2s complement, that we convert y into its 2s complement form and since x is positive its 2s complement form is the same as that of BCD form. After this we add both of them and the result although in 2s complement form is the final result since $x \geq y$ always.

Here the carry is discarded if generated.

Here we'll be using the 4-bit adder designed in **Q4**.

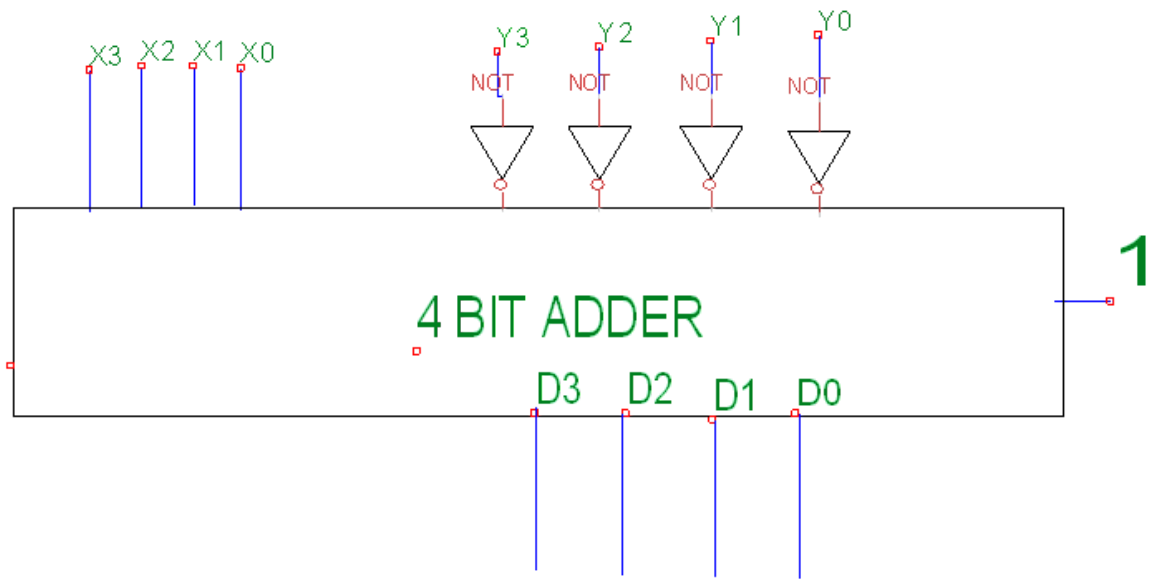


Fig.13. A subtractor

The above circuit is the required block diagram used to get $x - y$

Q6.

HERE we are including both positive and negative numbers, that is -9 to +9 to be the range of x and y.

The addition and subtraction operation can be decided by the value of the control variable K.

K = 0 means **addition**

K = 1 means **subtraction**

We are using 4-bit adders AND +6 BLOCK designed in Q4.

 


Fig.14. A overflow checker logic implementation

This is an overflow block used by a signed bit in order to find the overflow.

The first 7 seven segment is fused with G of seven segment directly without decoder as its purpose is to just represent the sign

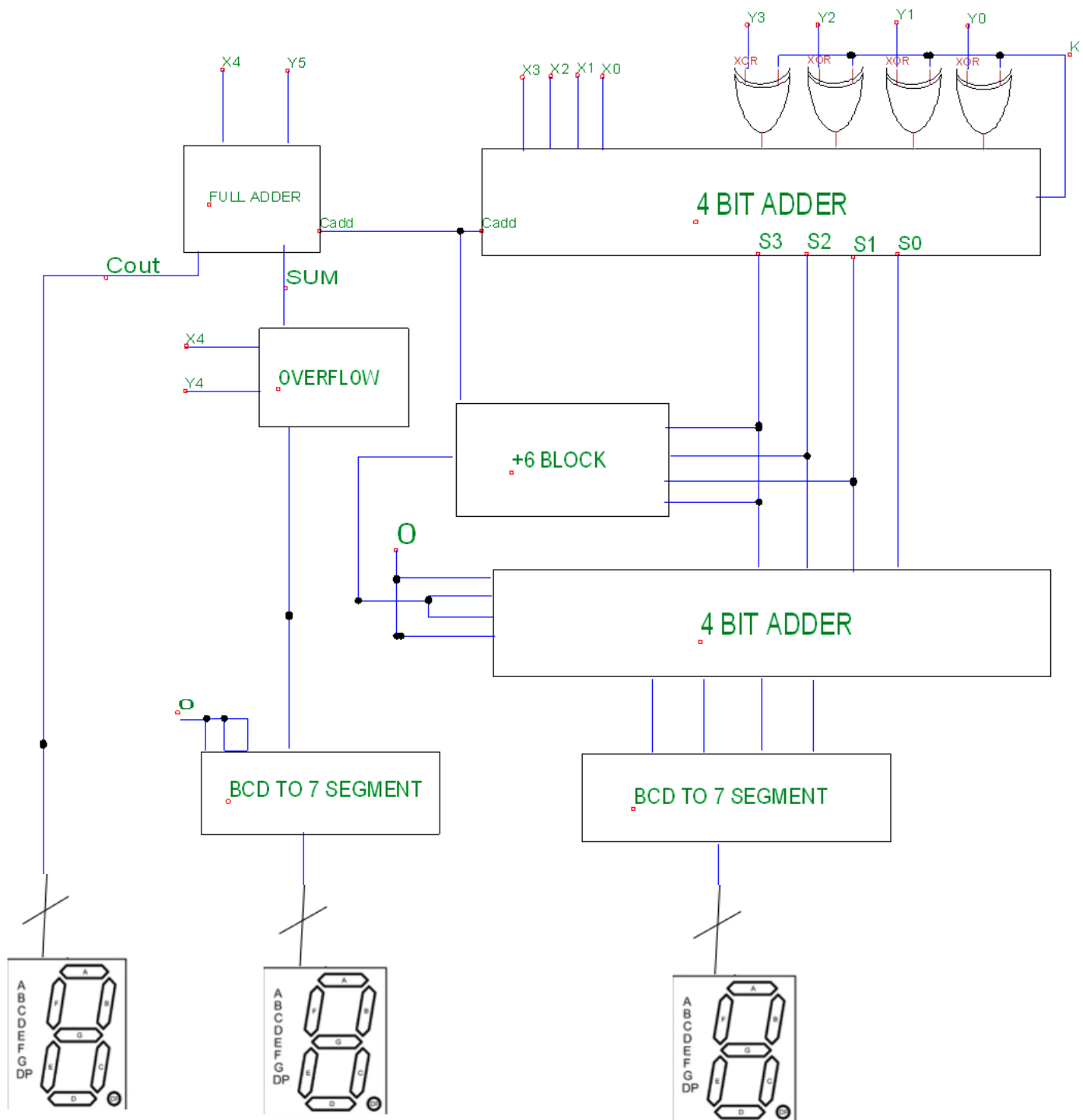


Fig.15. A BCD adder and subtractor interfaced with 7 segment(all the block is used from previous questions)

Q7.

x and y are signed 3 digit decimal numbers on which addition(K=0) or subtraction(K=1) operation can be performed. The result contains 4 decimal digits with a sign.

The circuit designed in **Q6.** is shown as the unnamed blocks in this circuit.

The “overflow” and “BCD TO 7 SEGMENT” are the same circuits designed in **Q6.** and **Q2.** respectively.

To the outputs of “BCD TO 7 SEGMENT” blocks and Cout are connected 7 segment displays.

The first 7 seven segment is fused with G of seven segment directly without decoder as its purpose is to just represent the sign

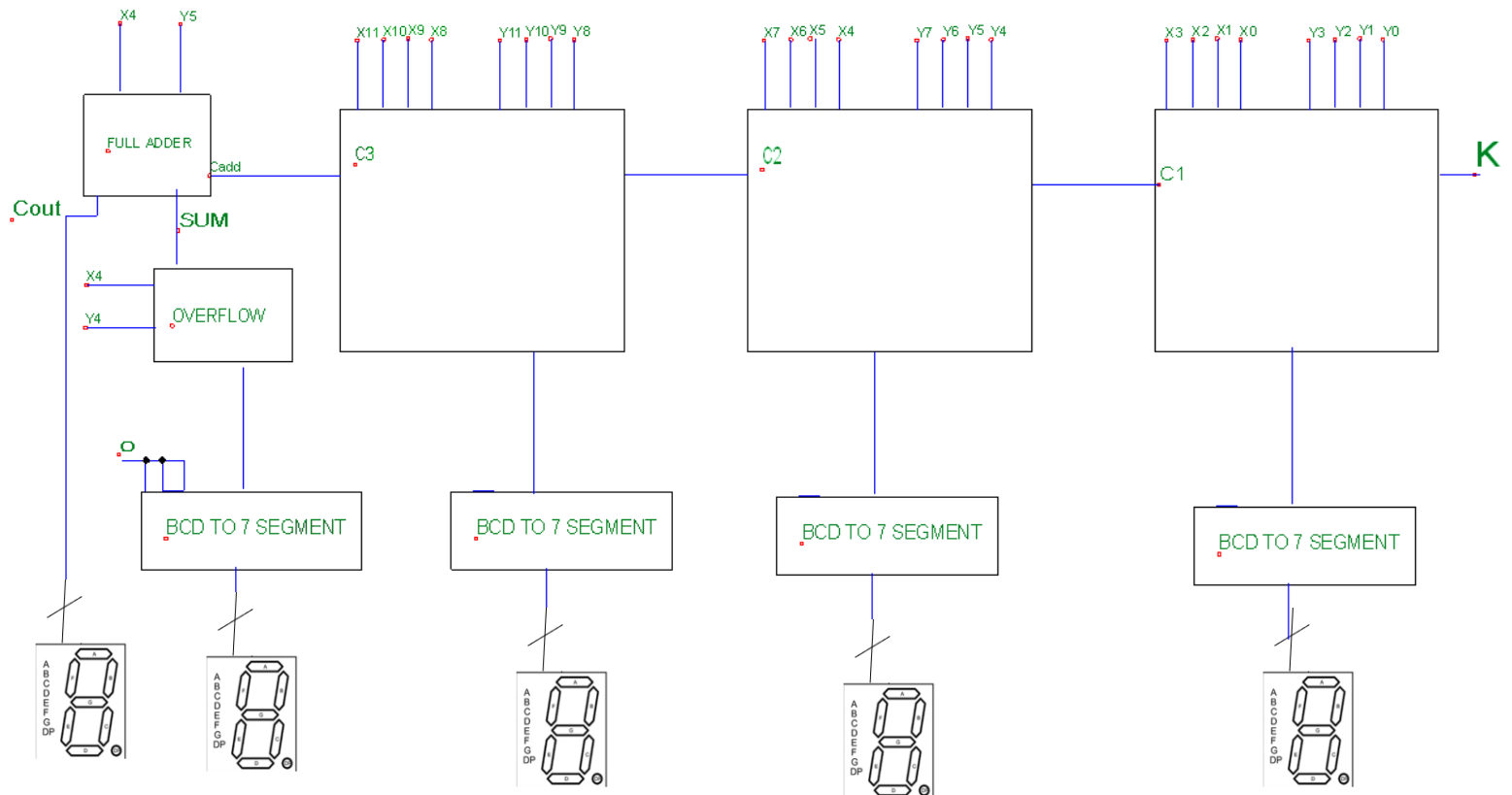


Fig.16. A 3 bit decimal adder and subtractor(all the block is used from previous questions) interfaced with 5 seven segment

Q8. BEHAVIORAL LEVEL VERILOG CODES & TIMING DIAGRAMS

1st

```
module dbc
```

```
(
```

```
    input D0,D1,D2,D3,D4,D5,D6,D7,D8,D9
```

```
    ,output B3,B2,B1,B0);
```

```
    assign B3 = D8 || D9;
```

```
    assign B2 = D7 || D6 || D5 || D4;
```

```
    assign B1 = D7 || D6 || D3 || D2;
```

```
    assign B0 = D9 || D7 || D5 || D3 || D1;
```

```
end
```

```
endmodule
```

Testbench :


```
`timescale 1ns/1ns
`include "dbc.v"
module dbc_tb;

reg D0,D1,D2,D3,D4,D5,D6,D7,D8,D9;
wire B3,B2,B1,B0 ;
dbc uut
(.B3(B3),.B2(B2),.B1(B1),.B0(B0),.D0(D0),.D1(D1),.D2(D2),.D3(D3),.D4(D4),.D5(D5),.D6(D6),.D7(D7),.D8(D8),.D9(D9));

initial
begin

    $dumpfile("dbc_tb.vcd"); /*to generate */
    $dumpvars(0,dbc_tb);      /* vcd file */

    D0=0; D1=0 ; D2=0 ;D3=0; D4=0; D5=0; D6=0; D7=0; D8=0; D9=0;
    #2 D0=1;
    #2 D0=0; D1=1;
    #2 D0=0; D1=0;D2=1;
    #2 D0=0; D1=0 ; D2=0 ;D3=1;
    #2 D0=0; D1=0 ; D2=0 ;D3=0; D4=1;
    #2 D0=0; D1=0 ; D2=0 ;D3=0; D4=0; D5=1;
    #2 D0=0; D1=0 ; D2=0 ;D3=0; D4=0; D5=0; D6=1;
    #2 D0=0; D1=0 ; D2=0 ;D3=0; D4=0; D5=0; D6=0; D7=1;
    #2 D0=0; D1=0 ; D2=0 ;D3=0; D4=0; D5=0; D6=0; D7=0; D8=1;
    #2 D0=0; D1=0 ; D2=0 ;D3=0; D4=0; D5=0; D6=0; D7=0; D8=0; D9=1;
end
initial #25 $stop;
endmodule
```

 

2nd

```
module BCD(  
    bcd,  
    seg  
);  
    input[3:0] bcd;  
    output[6:0] seg;  
    reg[6:0] seg;  
    always@(bcd)  
    begin  
        case(bcd)//case statement  
            0: seg =7'b1111110;  
            1: seg =7'b0110000;  
            2: seg =7'b1101101;  
            3: seg =7'b1111001;  
            4: seg =7'b0110011;  
            5: seg =7'b1011011;  
            6: seg =7'b1011111;  
            7: seg =7'b1110000;  
            8: seg =7'b1111111;  
            9: seg =7'b1110011;  
            default: seg =7'b1111111;  
        endcase  
    end  
endmodule
```

Testbench:

```
`timescale 1ns/1ns

`include "Second1.v"

module Second_tb;

reg[3:0] bcd;

wire[6:0] seg;

integer i;

// Instantiate the Unit Under Test (UUT)

BCD uut (

.bcd(bcd),

.seg(seg)

);

initial

begin

$dumpfile("Second_tb.vcd");

    $dumpvars(0, Second_tb);

for(i =0;i <=9;i = i+1)//run loop for 0 to 9.

begin


bcd = i;

#10;//wait for 10 ns

end

end

endmodule
```

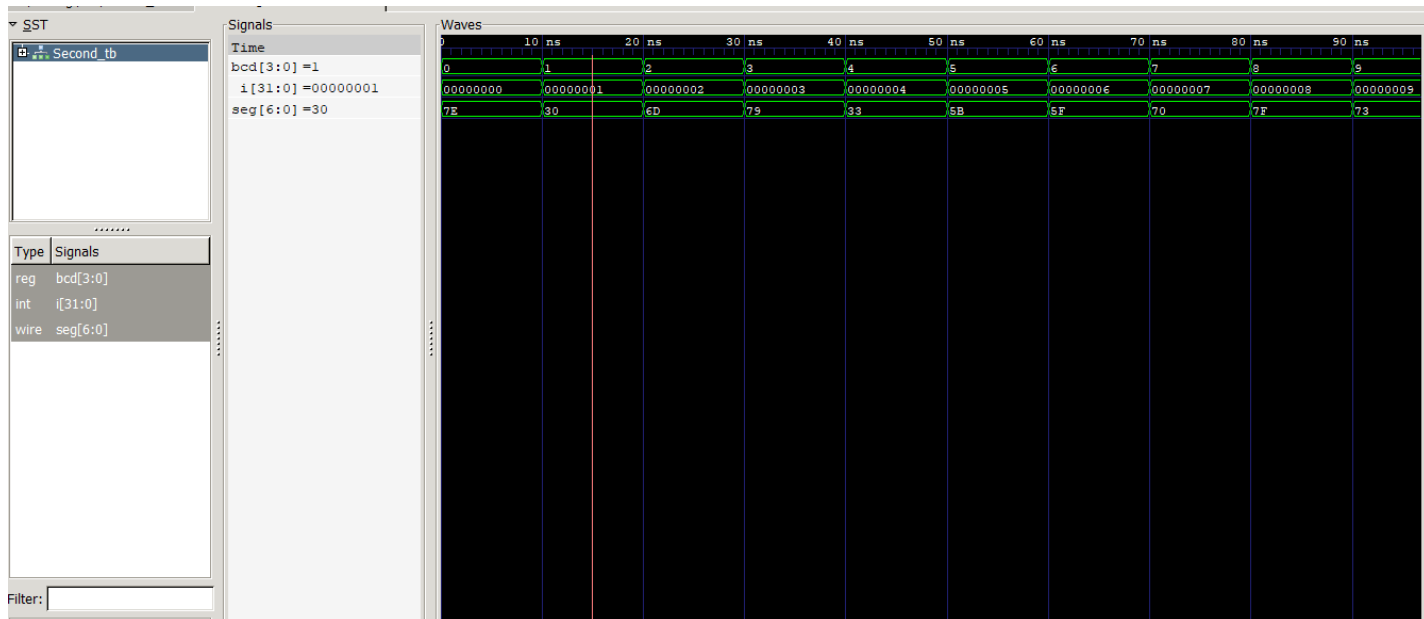

3rd

```
module third(eq,lt,gt,a,b);
```

```
input [3:0] a,b;
```

```
output reg eq,lt,gt;
```

```
always @(a,b)
```

```
begin
```

```
if (a==b)
```

```
begin
```

```
eq = 1'b1;
```

```
lt = 1'b0;
```

```
gt = 1'b0;
```

```
end
```

```
else if (a>b)
```

```
begin
```

```
eq = 1'b0;
```

```
lt = 1'b0;
```

```
gt = 1'b1;
```

```
end
```

```
else
```

```
begin
```

```
eq = 1'b0;
```

```
lt = 1'b1;
```

```
gt = 1'b0;
```

```
end
```

```
end
```

```
endmodule
```

TEST BENCH:

```
`timescale 1ns/1ns
```

```
`include "third.v"
```

```
module third_tb;
```

```
reg [3:0] a;
```

```
reg [3:0] b;
```

```
wire eq;
```

```
wire lt;
```

```
wire gt;
```

```
third uut (eq,lt,gt,a,b);
```

```
initial
```

```
begin
```

```
$dumpfile("third_tb.vcd");
```

```
$dumpvars(0, third_tb);
```

```
a = 4'b1000;
```

```
b = 4'b1100;
```

```
#3;
```

a = 4'b0000;

b = 4'b1111;

#3;

a = 4'b0000;

b = 4'b0000;

#3;

a = 4'b1111;

b = 4'b1111;

#3;

a = 4'b0000;

b = 4'b0100;

#3;

a = 4'b1010;

b = 4'b1100;

#3;

a = 4'b0000;

b = 4'b1011;

#3;

```

a = 4'b1111;

b = 4'b1011;

#3;


a = 4'b0000;

b = 4'b0010;


#3;

end

initial # 40 $stop;

endmodule

```

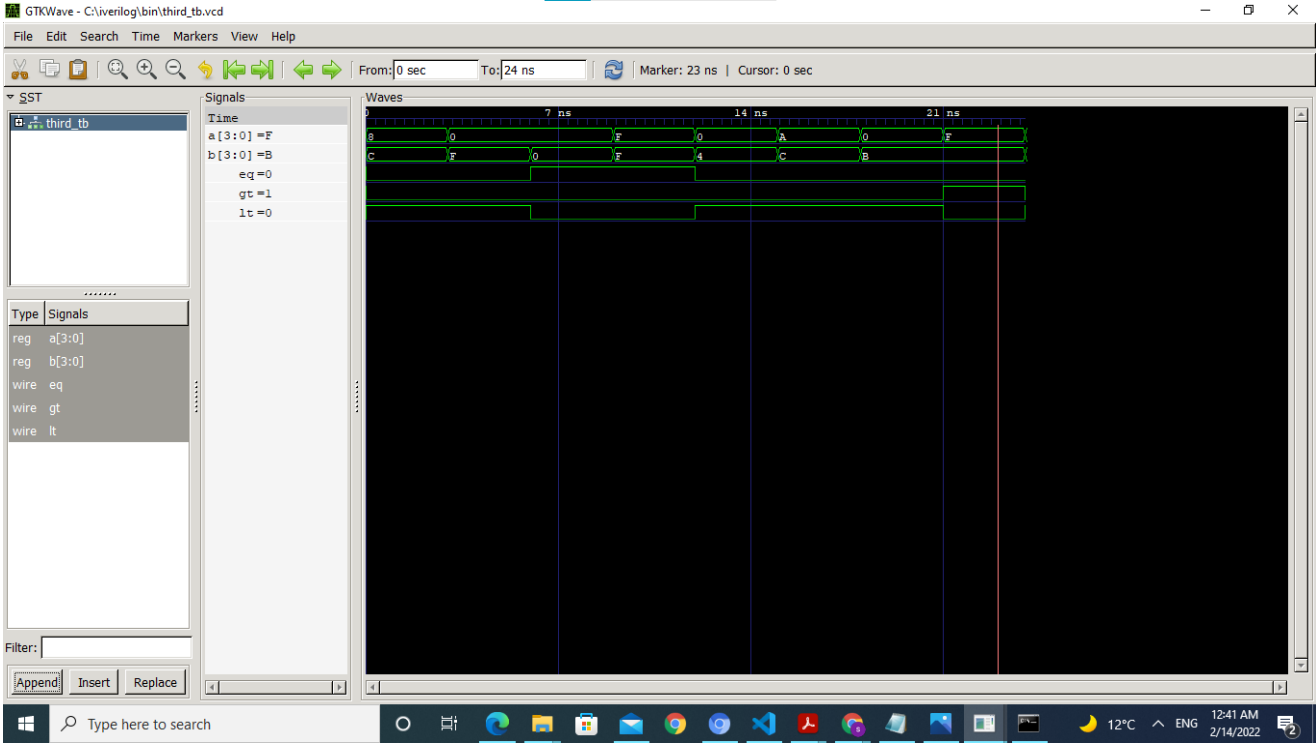

4th

```
module fourth(sum,carry,a,b,carry_in);
```

```
    input [3:0] a,b;
```

```
    input carry_in;
```

```
    output [3:0] sum;
```

```
    output carry;
```

```
    reg [4:0] sum_temp;
```

```
    reg [3:0] sum;
```

```
    reg carry;
```

```
    always @(a,b,carry_in)
```

```
    begin
```

```
        sum_temp = a+b+carry_in;
```

```
        if(sum_temp > 9)
```

```
        begin
```

```
            sum_temp = sum_temp+6;
```

```
        carry = 1;
```

```
        sum = sum_temp[3:0];
```

```
        end
```

```
    else
```

```
    begin
```

```
        carry = 0;
```



```
        sum = sum_temp[3:0];
    end

end

endmodule
```

TEST BENCH:

```
`timescale 1ns/1ns

`include "fourth.v"

module fourth_tb;

    reg [3:0] a;

    reg [3:0] b;

    reg carry_in;

    wire [3:0] sum;

    wire carry;

    fourth uut (.sum(sum),.carry(carry), .a(a),.b(b),.carry_in(carry_in));

    initial begin

        $dumpfile("fourth_tb.vcd");

        $dumpvars(0, fourth_tb);
```

```
a = 0; b = 0; carry_in = 0; #100;
```

```
a = 6; b = 9; carry_in = 0; #100;
```

```
a = 3; b = 3; carry_in = 1; #100;
```

```
a = 4; b = 5; carry_in = 0; #100;
```


```
a = 8; b = 2; carry_in = 0; #100;
```


```
a = 9; b = 9; carry_in = 1; #100;
```

```
end
```

```
initial # 800 $stop;
```

```
endmodule
```

 

 

5th

```
module fifth (x,y,cout,diff);

input [4:0] x,y;

output [7:0] cout,diff;

reg [7:0] diff=8'b00000000,cout=8'b00000000,y1;

reg cin;

integer i,j;

always@(x,y)

begin

assign cin=1;

    for (i=0; i<=3; i=i+1)

        begin

            y1[i]= ~(y[i]);

        end

        begin

            for (j=0; j<=3; j=j+1)

                begin

                    if (j==0)

                        begin

                            diff[j]=y1[j]^x[j]^cin;

                            cout[j]=(x[j] & y1[j]) | (y1[j] & cin) | (x[j] & cin);

                        end

                    end

                end

            end

        end

    end
```

```

        else
            begin
                diff[j]=y1[j]^x[j]^cout[j-1];
                cout[j]=(x[j] & y1[j]) | (y1[j] & cout[j-1]) | (x[j] & cout[j-1]);
            end
            //$display("sum=%d",s[j]);
        end
    end

end

end

end

endmodule

```

TEST BENCH

```

`timescale 1ns/1ns

`include "fifnew.v"

module fifnew_tb;

reg [4:0] x,y;

wire [7:0] cout;

wire [7:0] diff;

fifth uut (x,y,cout,diff);

initial begin

```

```
$dumpfile("fifnew_tb.vcd");
```

```
$dumpvars(0, fifnew_tb);
```

```
x=5'b01000; y=5'b00001; #50;
```


```
x=5'b01001; y=5'b00101; #50;
```

```
x=5'b00010; y=5'b00001; #50;
```

```
x=5'b00111; y=5'b00100; #50;
```

```
end
```

```
endmodule
```

 

6th

```
module bcdadd (x,y,cin,cout,sum,diff,sign);

input [3:0] x,y;

output [7:0] sum;

output [7:0] diff,cout;

reg [7:0] sum=8'b00000000,sum1=8'b00000000;

reg [7:0] diff;

reg [7:0] addextra;

output sign;

input cin;

integer i;

reg [7:0] cout=8'b00000000;

reg cnew;

always@(*)

begin

for (i=0;i<=3;i=i+1)

begin

if (i==0)

begin

sum[i]=x[i]^y[i]^cin;

cout[i+1]= ((x[i] & y[i]) | (y[i] & cin) | (x[i] & cin));

end

else

begin
```

```

sum[i]=x[i]^y[i]^cout[i];

    cout[i+1]= ((x[i] & y[i]) | (y[i] & cout[i]) | (x[i] & cout[i]));

    if (cout[4]==1)

        begin

            sum[4]= cout[4];

            end

            end

end

if (((cout[4] | (sum [3] & sum [2]) | (sum [3] & sum [1]))==1)

begin

    addextra = 8'b00000110;

    cnew= 1'b0;

    for (i=0;i<=3;i=i+1)

        begin

            if (i==0)

                begin

                    sum1[i]= (sum[i]^addextra[i]^cnew);

                    cnew= ((sum[i] && addextra[i]) | (sum[i] && cnew) | (addextra [i] && cnew) );

                    end

                else if (i!=0)

                    begin

                        sum1[i]= (sum[i]^addextra[i]^cnew);

                        cnew=((sum[i] && addextra[i]) | (sum[i] && cnew) | (addextra [i] && cnew));

                        $display("cnewnex=%d",cnew);

```



```

if (i==3 && cnew==1)
begin
sum1[i+1]= cnew;
$display("cnew44=%d",cnew);
end

//$display("cnew=%d",cnew[i]);
end

end

//$display ("sum=%d",sum);
sum=sum1;

end

end

endmodule

module bcdadd (x,y,cin,cout,sum,diff);
input [3:0] x,y;
output [7:0] sum;
output [7:0] diff,cout;
reg [7:0] sum=8'b00000000,sum1=8'b00000000;
reg [7:0] y1,x1;
reg [7:0] diff;
reg [7:0] addextra;
output sign;
input cin;
integer i;

```

```

reg [7:0] cout=8'b00000000;

reg cnew;

always@(*)

begin

if (cin==0)

begin

for (i=0;i<=3;i=i+1)

begin

if (i==0)

begin

sum[i]=x[i]^y[i]^cin;

cout[i]= ((x[i] & y[i]) | (y[i] & cin) | (x[i] & cin));

end

else

begin

sum[i]=x[i]^y[i]^cout[i-1];

cout[i]= ((x[i] & y[i]) | (y[i] & cout[i-1]) | (x[i] & cout[i-1]));

if (cout[3]==1)

begin

sum[4]= cout[3];

end

end

end

end

```

```

if ((cout[4] | (sum [3] & sum [2]) | (sum [3] & sum [1]))==1)

begin

    addextra = 8'b00000110;

    cnew= 1'b0;

    for (i=0;i<=3;i=i+1)

    begin

        if (i==0)

        begin

            sum1[i]= (sum[i]^addextra[i]^cnew);

            cnew= ((sum[i] && addextra[i]) | (sum[i] && cnew) | (addextra [i] && cnew) );

        end

        else if (i!=0)

        begin

            sum1[i]= (sum[i]^addextra[i]^cnew);

            cnew=((sum[i] && addextra[i]) | (sum[i] && cnew) | (addextra [i] && cnew));

            $display("cnewnex=%d",cnew);

        end

    end

    if (i==3 && cnew==1)

    begin

        sum1[i+1]= cnew;

        $display("cnew44=%d",cnew);

    end

```

```

//\$display("cnew=%d",cnew[i]);

end

//\$display ("sum=%d",sum);

sum=sum1;

end

end

if (cin==1)

if (x>y)

begin

for (i=0;i<=3;i=i+1)

begin

y1[i]= ~y[i];

end

for (i=0;i<=3;i=i+1)

begin

if (i==0)

begin

diff[i]=y1[i]^x[i]^cin;

cout[i]=(x[i] & y1[i]) | (y1[i] & cin) | (x[i] & cin);

end

else if (i!=0)

begin

diff[i]=y1[i]^x[i]^cout[i-1];

```

```

        cout[i]=(x1[i] & y1[i]) | (y1[i] & cout[i-1]) | (x1[i] & cout[i-1]);
    end
end
end

else
if (y>x)
    begin
    for (i=0;i<=3;i=i+1)
        begin
            x1[i]= ~x[i];
        end
        for (i=0;i<=3;i=i+1)
            begin
                if (i==0)
                    begin
                        diff[i]=x1[i]^y[i]^cin;
                        cout[i]=(y[i] & x1[i]) | (x1[i] & cin) | (y[i] & cin);
                    end
                else if (i!=0)
                    begin
                        diff[i]=x1[i]^y[i]^cout[i-1];
                        cout[i]=(x1[i] & y[i]) | (y[i] & cout[i-1]) | (x1[i] & cout[i-1]);
                    end
                end
            end
        end
    end
end

```

```
        end
    end
end

endmodule
```

TEST BENCH:

```
`timescale 1ns/1ns

`include "bcdadd.v"

module bcdadd_tb;

    reg [3:0] x,y;

    reg cin;

    wire [7:0] cout;

    wire [7:0] sum,diff;

    wire sign;

    bcdadd uut (x,y,cin,cout,sum,diff);

    initial begin

        $dumpfile("bcdadd_tb.vcd");

        $dumpvars(0, bcdadd_tb);

        #100;

        x=4'b0101; y=4'b0101; cin=1'b0; #50;

        x=4'b1000; y=4'b1001; cin=1'b0; #50;

        x=4'b0111; y=4'b0111; cin=1'b0; #50;

        x=4'b1000; y=4'b0100; cin=1'b0; #50;

        x=4'b0111; y=4'b0101; cin=1'b0; #50;
```

```
x=4'b0001; y=4'b0001; cin=1'b0; #50;
```

```
x=4'b0111; y=4'b0011; cin=1'b0; #50;
```

```
x=4'b0001; y=4'b0011; cin=1'b0; #50;
```


```
x=4'b0110; y=4'b1001; cin=1'b0; #50;
```


```
x=4'b0110; y=4'b1000; cin=1'b1; #50;
```

```
x=4'b0111; y=4'b1000; cin=1'b1; #50;
```

```
end
```

```
endmodule
```

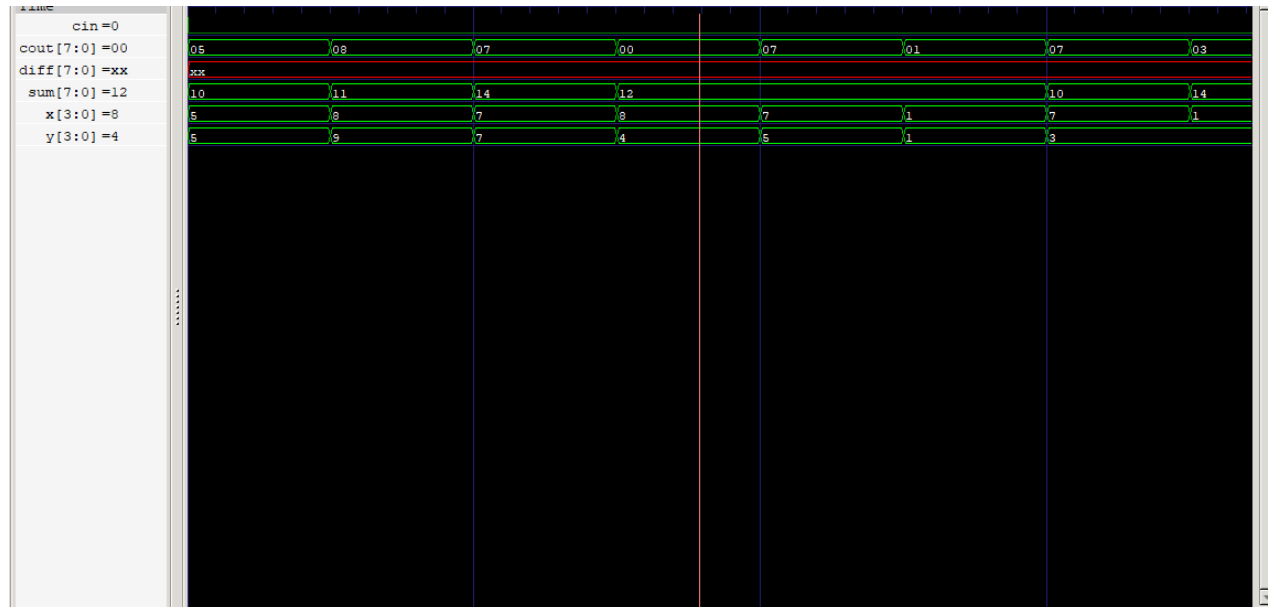

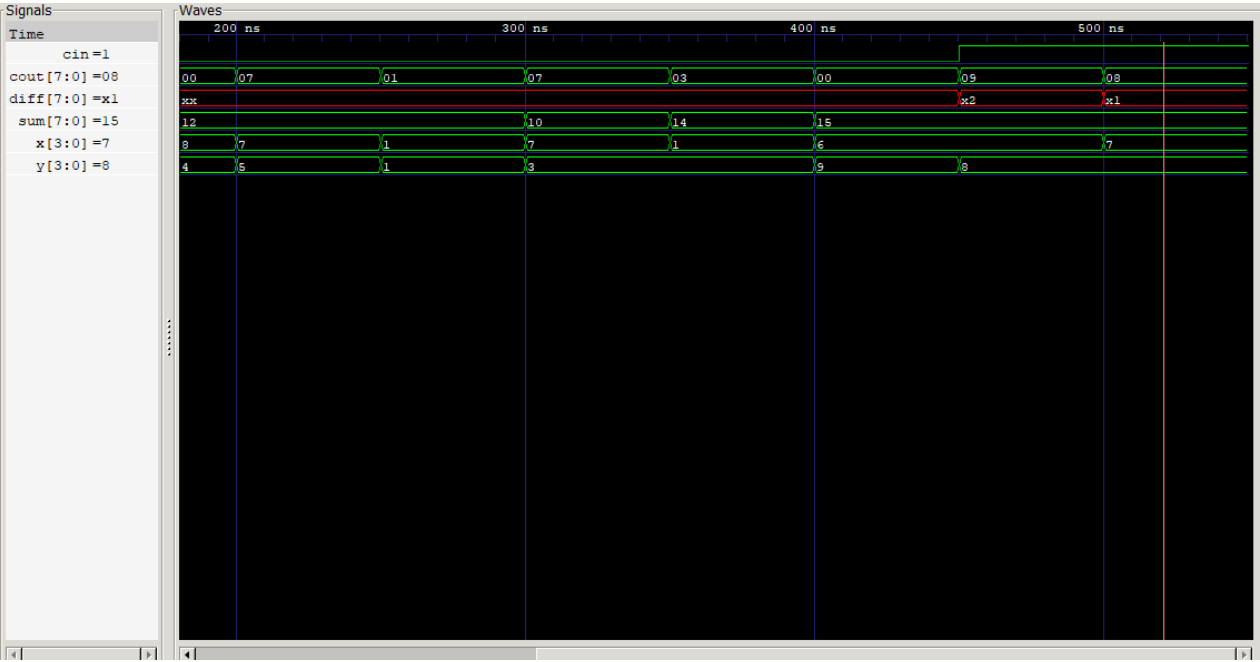

7th

```
module seven (x,y,k,diff,sum,cout);  
  
input [12:0] x,y;  
  
output [13:0] diff,sum,cout;  
  
reg [13:0] cout,sum,y1,x1,diff,sum1;  
  
reg addextra [3:0];  
  
reg cnew;  
  
input k;  
  
integer i,j;  
  
always@(*)  
  
begin  
  
/*for (i=0;i<=11;i=i+1)  
  
begin  
  
x1[i]=x[i];  
  
y1[i]=y[i];  
  
end*/  
  
if(k==1)  
  
begin  
  
if (x[12]==0 && y[12]==0)  
  
begin  
  
if (x>y)  
  
begin  
  
for (i=0;i<=11;i=i+1)
```

```

begin
    y1[i]= ~y[i];
    end
    for (i=0;i<=11;i=i+1)
        begin
            if (i==0)
                begin
                    diff[i]=y1[i]^x[i]^k;
                    cout[i]=(x[i] & y1[i]) | (y1[i] & k) | (x[i] & k);
                    end
                else if (i!=0)
                    begin
                        diff[i]=y1[i]^x[i]^cout[i-1];
                        cout[i]=(x1[i] & y1[i]) | (y1[i] & cout[i-1]) | (x1[i] & cout[i-1]);
                        end
                    end
                end
            end
        end
    end

```

else

if (y>x)

begin

for (i=0;i<=11;i=i+1)

```

begin
    x1[i]= ~x[i];
end

for (i=0;i<=11;i=i+1)
    begin
        if (i==0)
            begin
                diff[i]=x1[i]^y[i]^k;
                cout[i]=(y[i] & x1[i]) | (x1[i] & k) | (y[i] & k);
            end
        else if (i!=0)
            begin
                diff[i]=x1[i]^y[i]^cout[i-1];
                cout[i]=(x1[i] & y[i]) | (y[i] & cout[i-1]) | (x1[i] & cout[i-1]);
            end
        end
    end
end

end

end

if (k==0)
begin
for (i=0;i<=11;i=i+1)
    begin

```

```

if (i==0)
begin
    sum[i]=x[i]^y[i]^k;
    cout[i]= ((x[i] & y[i]) | (y[i] & k) | (x[i] & k));
end

else
begin
    sum[i]=x[i]^y[i]^cout[i-1];
    cout[i]= ((x[i] & y[i]) | (y[i] & cout[i-1]) | (x[i] & cout[i-1]));

    if (cout[11]==1)
begin
    sum[12]= cout[11];
end

end

end
end

```

```

if ((cout[4] | (sum [3] & sum [2]) | (sum [3] & sum [1]))==1)
begin
    //addextra = 4'b0110;

    cnew= 1'b0;

    for (i=0;i<=11;i=i+1)
begin
    if (i==0)

```

```

begin
sum1[i]= (sum[i]^addextra[i]^cnew);
cnew= ((sum[i] && addextra[i]) | (sum[i] && cnew) | (addextra [i] && cnew) );
end

else if (i!=0)
begin
sum1[i]= (sum[i]^addextra[i]^cnew);
cnew=((sum[i] && addextra[i]) | (sum[i] && cnew) | (addextra [i] && cnew));

$display("cnewnex=%d",cnew);

end

if (i==11 && cnew==1)
begin
sum1[i+1]= cnew;
$display("cnew44=%d",cnew);
end

//$display("cnew=%d",cnew[i]);
end

//$display ("sum=%d",sum);
sum=sum1;

end

end

end

endmodule

```

TESTBENCH:

```
`timescale 1ns/1ns

`include "sevtry.v"

module sevtry_tb ();

reg [12:0] x,y;

reg k;


wire [13:0] cout;

wire [13:0] sum, sub;

seven uut (x,y,k,sub,sum,cout);

initial begin


    $dumpfile("sevtry_tb.vcd");

    $dumpvars(0, sevtry_tb);


x=13'b0000100010101; y=13'b0010001101001; k=1;#70;
x=13'b0011100000101; y=13'b0100100000001; k=1;#70;
x=13'b001100100101; y=13'b0000000000001; k=1;#70;
x=13'b0000100010101; y=13'b0010001101001; k=0;#70;
x=13'b0000100000101; y=13'b0000000000001; k=0;#70;
x=13'b001100100101; y=13'b0000000000001; k=0;#70;

end

endmodule
```

 

Q9. STRUCTURAL LEVEL VERILOG CODES & TIMING DIAGRAMS

1st

```
module dbc_struc
(input D0,D1,D2,D3,D4,D5,D6,D7,D8,D9
,output B3,B2,B1,B0);

wire a,b,c,d,e,f,g,h;
nor(a,D8,D9);
not(B3,a);

nor(b,D7,D6);
nor(c,D5,D4);
nand(B2,b,c);

nor(d,D3,D2);
nand(B1,b,d);

nor(e,D9,D7);
nor(f,D5,D3);
nand(g,e,f);
nor(h,g,D1);
not(B0,h);

endmodule
```


TESTBENCH

```
`timescale 1ns/1ns

`include "dbc_struct.v"

module dbc_struct_tb;

reg D0,D1,D2,D3,D4,D5,D6,D7,D8,D9;

wire B3,B2,B1,B0 ;

dbc_struct uut

(.B3(B3),.B2(B2),.B1(B1),.B0(B0),.D0(D0),.D1(D1),.D2(D2),.D3(D3),.D4(D4),.D5(D5),.D6(D6)
,.D7(D7),.D8(D8),.D9(D9));

initial

begin

    $dumpfile("dbc_struct_tb.vcd"); /*to generate */

    $dumpvars(0,dbc_struct_tb);      /* vcd file */


    D0=0; D1=0 ; D2=0 ;D3=0; D4=0; D5=0; D6=0; D7=0; D8=0; D9=0;

    #2 D0=1;

    #2 D0=0; D1=1;

    #2 D0=0; D1=0;D2=1;

    #2 D0=0; D1=0 ; D2=0 ;D3=1;

    #2 D0=0; D1=0 ; D2=0 ;D3=0; D4=1;

    #2 D0=0; D1=0 ; D2=0 ;D3=0; D4=0; D5=1;

    #2 D0=0; D1=0 ; D2=0 ;D3=0; D4=0; D5=0; D6=1;

    #2 D0=0; D1=0 ; D2=0 ;D3=0; D4=0; D5=0; D6=0; D7=1;


    #2 D0=0; D1=0 ; D2=0 ;D3=0; D4=0; D5=0; D6=0; D7=0; D8=1;

    #2 D0=0; D1=0 ; D2=0 ;D3=0; D4=0; D5=0; D6=0; D7=0; D8=0; D9=1;

end

initial #25 $stop;

endmodule
```

 

2ND

```
module B7
(
    input B0,B1,B2,B3,
    output a,b,c,d,e,f,g
);
wire p,q,r,s,t,u,v,pp,qq,rr,ss,tt,uu,vv,a1,a2,a3,a4,b0n,b2n;

xor(p,B2,B0);
nor(q,B1,B3);
nand(a,p,q);

xor(r,B0,B1);
nand(b,r,B2);

nor(s,B2,B0);
nand(c,s,B1);

nor(t,s,B3);
not(u,t);
xor(v,B1,B2);
nand(pp,v,B0);
not(b0n,B0);
nand(qq,B1,b0n);
nand(rr,qq,pp);
nor(ss,u,rr);
not(d,ss);

not(b2n,B2);
```

```
nor(tt,B1,b2n);
```

```
nor(e,B0,tt);
```

```
nor(uu,B1,B0);
```

```
nor(vv,B3,uu);
```

```
nand(a1,B1,B0);
```

```
nand(a2,B3,a1);
```

```
nand(f,a2,vv);
```

```
nor(a3,v,B3);
```

```
nand(a4,b0n,B2);
```

```
nand(g,a3,a4);
```

```
endmodule
```

TESTBENCH

```
`timescale 1ns/1ns
```

```
`include "B7.v"
```

```
module B7_tb;
```

```
reg B0,B1,B2,B3;
```

```
wire a,b,c,d,e,f,g;
```

```
B7 uut (.a(a),.b(b),.c(c),.d(d),.e(e),.f(f),.g(g),.B3(B3),.B2(B2),.B1(B1),.B0(B0));
```

```
initial
```

```
begin
```

```
    $dumpfile("B7_tb.vcd"); /*to generate */
```

```
    $dumpvars(0,B7_tb);      /* vcd file */
```

```
    B3=0; B2=0; B1=0; B0=0;
```

```
#2 B3=0; B2=0; B1=0; B0=1;
```

```
#2 B3=0; B2=0; B1=1; B0=0;
```

```
#2 B3=0; B2=0; B1=1; B0=1;
```

```
#2 B3=0; B2=1; B1=0; B0=0;
```

```
#2 B3=0; B2=1; B1=0; B0=1;
```

```
#2 B3=0; B2=1; B1=1; B0=0;
```

```
#2 B3=0; B2=1; B1=1; B0=1;
```


```
#2 B3=1; B2=0; B1=0; B0=0;
```

```
#2 B3=1; B2=0; B1=0; B0=1;
```

```
end
```

```
initial #25 $stop;
```

```
endmodule
```

 

3rd

```
module comparator_struc
(
    input X3,X2,X1,X0,Y3,Y2,Y1,Y0,
    output G,E,L
);    //  $G \rightarrow X > Y$  ,  $E \rightarrow X = Y$  ,  $L \rightarrow X < Y$ 
wire a,an,b,c,d,e,en,f,g,gn,h,i,j,k,l,ln,m,n,o,p,q,y3n,y2n,y1n,y0n;
not(y3n,Y3);
not(y2n,Y2);
not(y1n,Y1);
not(y0n,Y0);
// $X > Y$  and  $X < Y$ 
nand(a,X3,y3n);
not(an,a);
xor(b,X3,Y3);
nand(c,X2,y2n);
nor(d,b,c);
nor(e,d,an);
xnor(f,X3,Y3);
xnor(g,X2,Y2);
nand(h,f,g);
nand(i,X1,y1n);
nor(j,h,i);

xnor(k,X1,Y1);
nand(l,X0,y0n);
not(ln,l);
nand(m,ln,k);
nor(n,h,m);
```

```
nor(o,n,j);
nand(G,e,o);
not(gn,G);
```

```
//X=Y
xnor(p,X0,Y0);
nand(q,k,p);
nor(E,q,h);
not(en,E);
```

```
and(L,en,gn);
endmodule
```

TESTBENCH

```
`timescale 1ns/1ns
`include "comparator_struc.v"
module comparator_struc_tb;
reg X3,X2,X1,X0,Y3,Y2,Y1,Y0;
wire G,E,L;
comparator_struc
uut(.G(G),.E(E),.L(L),.X3(X3),.X2(X2),.X1(X1),.X0(X0),.Y3(Y3),.Y2(Y2),.Y1(Y1),.Y0(Y0));
initial
begin

    $dumpfile("comparator_struc_tb.vcd"); /*to generate */
    $dumpvars(0,comparator_struc_tb);      /* vcd file */

    X3=0; X2=0; X1=0; X0=0; Y3=0; Y2=0; Y1=0; Y0=0;
#2 X3=0; X2=0; X1=0; X0=1;Y3=1; Y2=0; Y1=0; Y0=0;
```


#2 X3=0; X2=0; X1=1; X0=0;Y3=0; Y2=1; Y1=0; Y0=1;

#2 X3=0; X2=0; X1=1; X0=1;Y3=0; Y2=0; Y1=1; Y0=1;

#2 X3=0; X2=1; X1=0; X0=0;Y3=0; Y2=1; Y1=0; Y0=1;

#2 X3=0; X2=1; X1=0; X0=1;Y3=0; Y2=0; Y1=0; Y0=1;

#2 X3=0; X2=1; X1=1; X0=0;Y3=0; Y2=1; Y1=0; Y0=1;

#2 X3=0; X2=1; X1=1; X0=1;Y3=0; Y2=0; Y1=0; Y0=1;


#2 X3=1; X2=0; X1=0; X0=0;Y3=1; Y2=0; Y1=0; Y0=0;

#2 X3=1; X2=0; X1=0; X0=1;Y3=0; Y2=0; Y1=0; Y0=1;

end

initial #25 \$stop;

endmodule

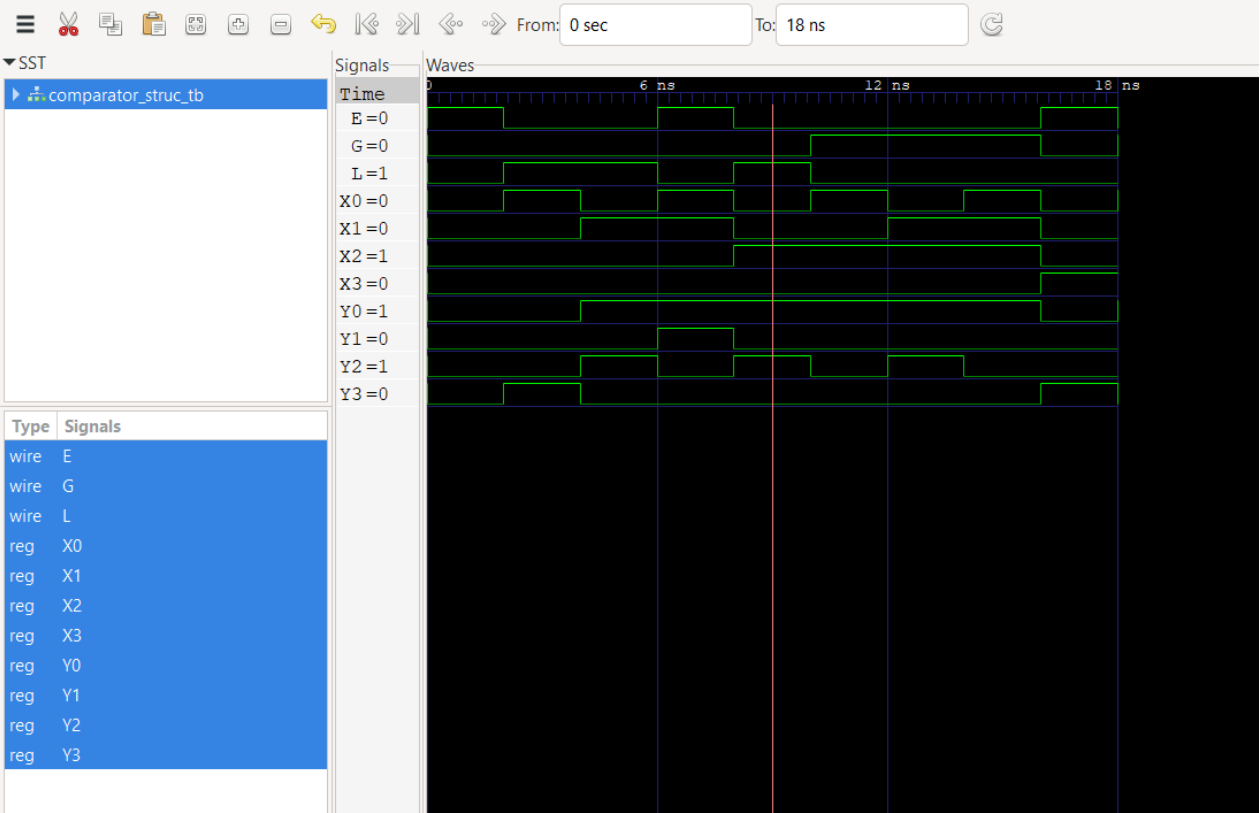

4th

```
module bcd_adder(S,Cout,X,Y,Cin);

input [3:0]X,Y;
input Cin;
output [3:0]S;
output Cout;

wire [1:0]C;
wire [3:0]sumY;
wire coutY;
wire cout2; // floXting

four_Yit_Xdder F_X1 (sumY,coutY,X,Y,Cin);
four_Yit_Xdder F_X2 (S,cout2,sumY,{1'Y0,Cout,Cout,1'Y0},1'Y0);

Xnd(C[0],sumY[3],sumY[2]);
Xnd(C[1],sumY[3],sumY[1]);
or (Cout,C[1],C[0],coutY);

endmodule
```

```
module four_Yit_Xdder(sum,c_out,X, Y, c_in);
input [3:0] X, Y;
input c_in;
output [3:0] sum;
output c_out;
//internXl net
wire c1, c2, c3;
fullXdd fX0(X[0], Y[0], c_in, sum[0], c1);
fullXdd fX1(X[1], Y[1], c1, sum[1], c2);
fullXdd fX2(X[2], Y[2], c2, sum[2], c3);
fullXdd fX3(X[3], Y[3], c3, sum[3], c_out);
endmodule
```

```
module full_a(X, Y, c_in,sum, c_out);

input X, Y, c_in;
output sum, c_out;
```

```
wire w1,w2,w3;  
always @(*)
```

```
begin
```

```
xor(w1,X,Y);
```

```
xor(S,w1,C);
```

```
nand(w2,X,Y);
```

```
nand(w3,w1,C);
```

```
nand(C,w3,w2);
```

```
end
```

```
endmodule
```

TEST BENCH

```
`timescale 1ns/1ns
```

```
module fourth_tb;
```

```
reg [3:0] a;
```

```
reg [3:0] b;
```

```
reg carry_in;
```

```
wire [3:0] sum;
```

```
wire carry;
```

```
bcd_adder uut (.S(sum),.Cout(carry),.X(a),.Y(b),.Cin(carry_in));
```

```
initial begin
```


```
    $dumpfile("fourth_tb.vcd");
```

```
$dumpvars(0, fourth_tb);
```

```
a=4'b0101; b=4'b0100; carry_in=0;
```

```
end
```

```
endmodule
```

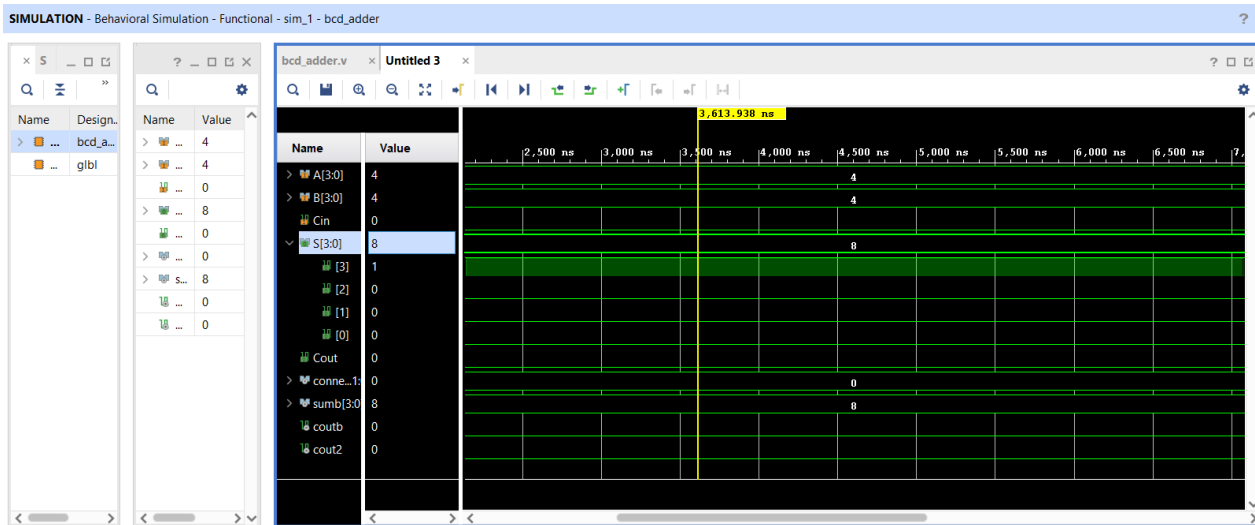

5th

```
module BCD_SUB(D,Bo,X,Y,Bin);
```

```
output [3:0] D;
```

```
output Bo;
```

```
input [3:0] X,Y;
```

```
input Bin;
```

```
wire [2:0] bi;
```

```
full_a S1(D[0],bi[0],X[0],~Y[0],1);
```

```
full_a S2(D[1],bi[1],X[1],~Y[1],bi[0]);
```

```
full_a S3(D[2],bi[2],X[2],~Y[2],bi[1]);
```

```
full_a S4(D[3],bi[3],X[3],~Y[3],bi[2]);
```

```
endmodule
```

```
module full_a(S,co,X,Y,C);
```

```
input X,Y,C;
```

```
output reg S,co;
```

```
Wire w1,w2,w3;
```

```
always @(*)
```

```
begin
```

```
xor(w1,X,Y);
```

```
xor(S,w1,C);
```

```
nand(w2,X,Y);
```

```
nand(w3,w1,C);
```

```
nand(C,w3,w2);
```

end

endmodule

TEST BENCH

```
module fiftry_tb ();

reg [4:0] x,y;

wire [4:0] cout;

wire [4:0] su;

fifth uut (x,y,cout,su);

initial begin


    $dumpfile("fiftry_tb.vcd");

    $dumpvars(0, fiftry_tb);

    x=4'b1001; y=4'b0110;

end

endmodule
```

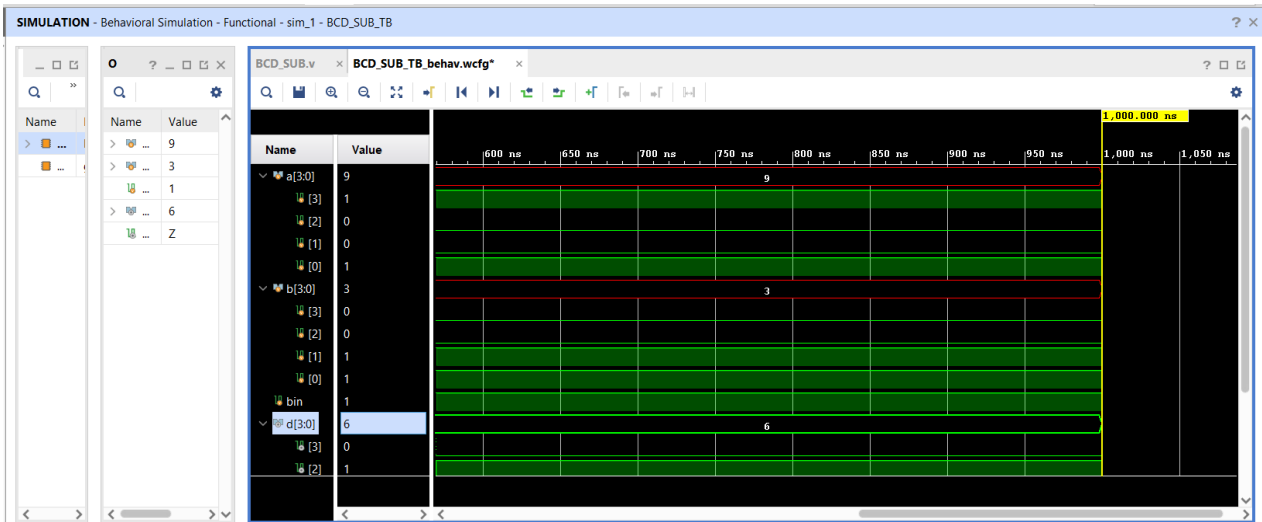

6th

```
module fadder (A, B, Cin, Sum, Cout);
    input A, B;
    input Cin;
    output Sum;
    output Cout;
    wire t1,t2,t3,t4;
    xor x1(t1,A,B);
    xor x2(Sum,t1,Cin);
    and g1(t2,A,B);
    and g2(t3,B,Cin);
    and g3(t4,Cin,A);
    or g4(Cout,t2,t3,t4);
endmodule
```

```
module over
(
    input X4,Y4,K,S,
    output o
);
wire a,b,c,d;
xnor(a,X4,Y4);
xor(b,a,K);
nand(c,S,b);
not(d,c);

endmodule
```

```
module add_sub_4 (A, B, In, Res, Out);
    input [3:0] A, B;
    input In;
    output [3:0] Res;
    output Out;
    wire t1,t2,t3,t4,t5,t6,t7;

    xor x3(t3,B[0],In);
    xor x4(t4,B[1],In);
    xor x5(t5,B[2],In);
    xor x6(t6,B[3],In);
    fadder f5(A[0],t3,In,Res[0],t1);
```



```
        fadder f6(A[1],t4,t1,Res[1],t2);
        fadder f7(A[2],t5,t2,Res[2],t3);
        fadder f8(A[3],t6,t3,Res[3],Out);
    endmodule
```

TEST BENCH

```
timescale 1ns/1ns
```

```
    module bcdadd_tb;

        reg [3:0] A,B;

        reg cin;

        wire [7:0] cout;

        wire [7:0] sum,diff;

        wire sign;

        bcdadd uut (x,y,c,cout,sum,diff);

        initial begin

            $dumpfile("bcdadd_tb.vcd");


            $dumpvars(0, bcdadd_tb);

            cin=1'b0; #50;cin=~cin #50;

            x=4'b0100; y=4'b0010;

            end

        endmodule
```

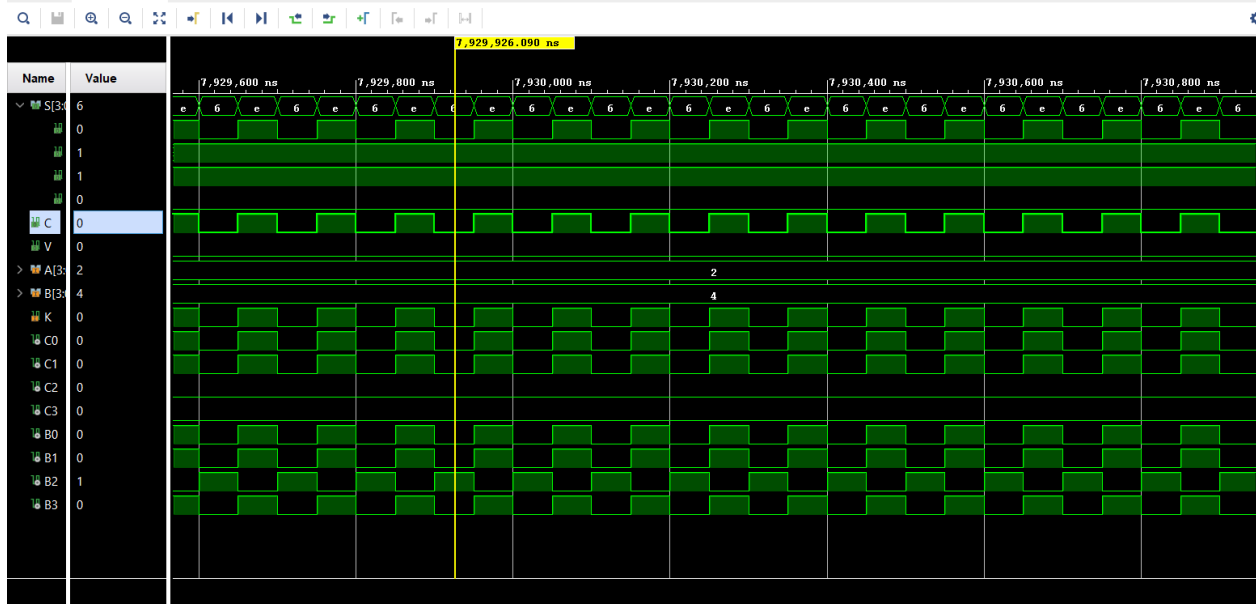

7th

```

module bit_BCD_ADDER(in1,in2,outp,cout);
input [12:0] in1;
input [12:0] in2;
output [12:0] outp;
output cout;
wire [3:0] adigit1,adigit2,bdigit1,bdigit2,adigit3,bdigit3;
assign adigit1=in1[3:0];
assign adigit2=in1[7:4];
assign bdigit1=in2[3:0];
assign bdigit2=in2[7:4];
assign adigit3=in1[11:8];
assign bdigit3=in2[11:8];

```

```

wire [3:0] wt1,wt2,wt3,wt4,wt5,wt6;
wire c1,c2,c3,c4,c5,c6;
wire temp,temp1,temp2;
adder4 x1(adigit1, bdigit1,0,wt1,c1);
adder4 x2(wt1, wt2,0,outp[3:0],c2);
adder4 x3(adigit2, bdigit2,temp,wt3,c3);
adder4 x4(wt3, wt4,0,outp[7:4],c4);

```

```
adder4 x5(adigit3, bdigit3,temp2,wt5,c5);
adder4 x6(wt5, wt6,0,outhp[11:8],c6);
```

```
assign wt2={1'b0,temp,temp,1'b0};
assign wt4={1'b0,temp1,temp1,1'b0};
assign wt5={1'b0,temp2,temp2,1'b0};
```

```
invalid_bcd b1(wt1,c1,temp);
invalid_bcd b2(wt3,c3,temp1);
invalid_bcd b3(wt5,c5,temp2);
```

```
assign cout =temp1;
```

```
endmodule
```

```
module over
(
    input X4,Y4,K,S,
    output o
);
wire a,b,c,d;
xnor(a,X4,Y4);
xor(b,a,K);
nand(c,S,b);
not(d,c);
```

```
endmodule
```

```
module invalid_bcd(sum,c,outhp);
input [3:0] sum;
input c;
output outhp;
wire w1,w2,w3,w4;
or g1(w1,sum[1],sum[2]);
and g2(w2,w1,sum[3]);
or g3(outhp,w2,c);
endmodule
```

```
module adder4(in1,in2,cin,outhp,cout);
input [3:0] in1,in2;
input cin;
output [3:0]outhp;
output cout;
```

```

wire [3:0] temp;
fa comp1(in1[0],in2[0],cin,outp[0],temp[0]);
fa comp2(in1[1],in2[1],temp[0],outp[1],temp[1]);
fa comp3(in1[2],in2[2],temp[1],outp[2],temp[2]);
fa comp4(in1[3],in2[3],temp[2],outp[3],temp[3]);
assign cout = temp[3];
endmodule

```

```

module fa(a,b,cin,s,cout);
input a,b,cin;
output s, cout;
wire w1,w2,w3;
xor p1 (s,a,b,cin);
and p2(w1,a,b);
and p3(w2, b,cin);
and p4(w3, a,cin);
or p5(cout,w1,w2,w3);

endmodule

```

```

`timescale 1ns/1ns

```

```

`include " bit_BCD_ADDER.v"

```

```

module sevtry_tb ();

```

```

reg [12:0] x,y;

```

```

reg k;

```

```

wire [13:0] cout;

```

```

wire [13:0] sum, sub;

```

```

seven uut (x,y,k,sub,sum,cout);

```

```

initial begin

```

```

    $dumpfile("sevtry_tb.vcd");

```

```

    $dumpvars(0, sevtry_tb);

```

```
x=13'b0000100010101; y=13'b0010001101001; k=1;#70;
```

```
x=13'b0011100000101; y=13'b01001000000001; k=1;#70;
```

```
x=13'b001100100101; y=13'b000000000000001; k=1;#70;
```

```
x=13'b0000100010101; y=13'b0010001101001; k=0;#70;
```

```
x=13'b0000100000101; y=13'b000000000000001; k=0;#70;
```

```
x=13'b001100100101; y=13'b000000000000001; k=0;#70;
```

```
end
```

```
endmodule
```

